

# Quantum Circuits


---

A formal way to represent protocols such as superdense coding, and the basis for defining quantum complexity classes

Slides are based on John Watrous' lectures 3 and 7

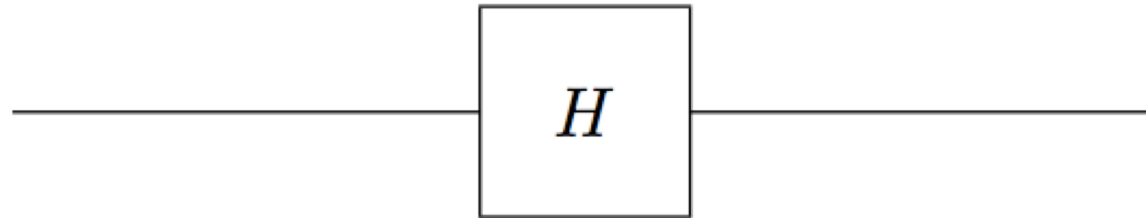
# Quantum circuits by example

- A Hadamard transform on a single superposition



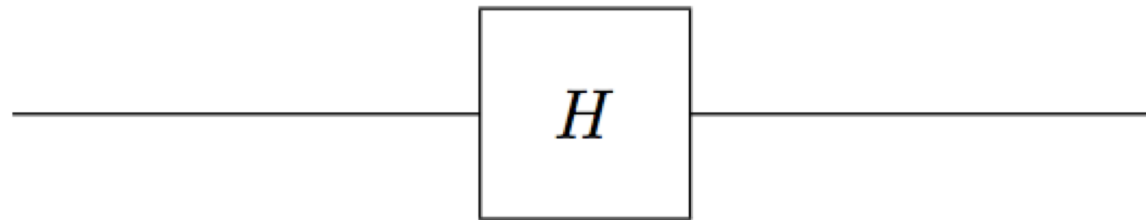
# Quantum circuits by example

- A Hadamard transform on a single superposition




- A Hadamard transform on input  $\frac{1}{\sqrt{2}} |0\rangle - \frac{1}{\sqrt{2}} |1\rangle$

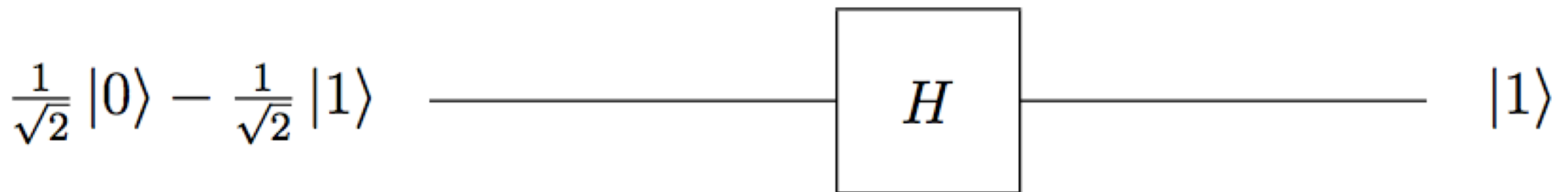

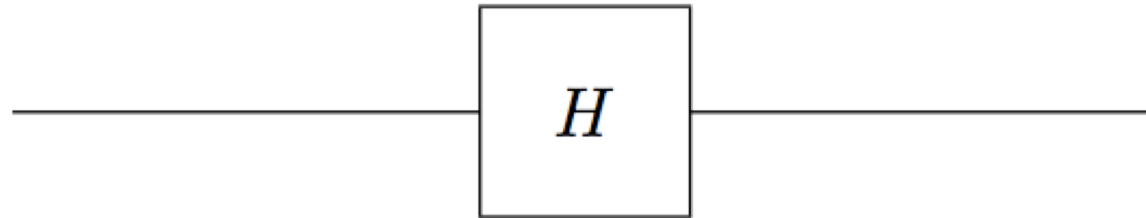
# Quantum circuits by example

- A Hadamard transform on a single superposition



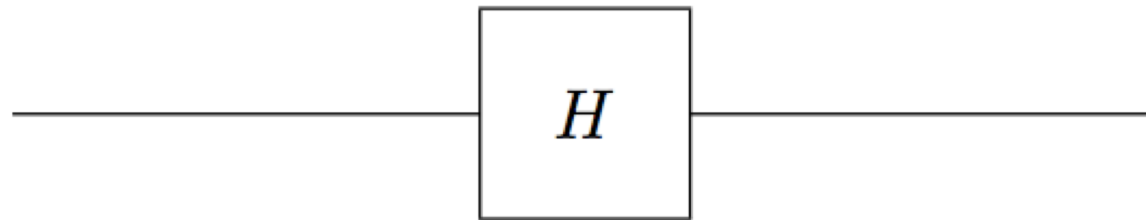
# Quantum circuits by example

- A Hadamard transform on a single superposition




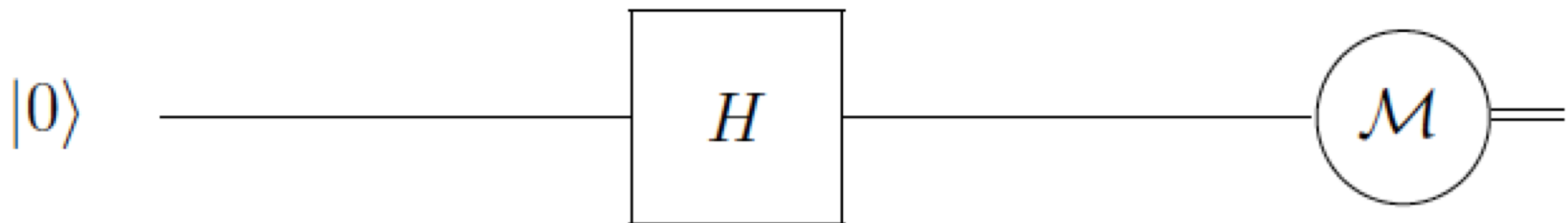- A measurement produces a classical bit (represented by double lines)




# Quantum circuits by example

- A NOT operation with classical input 0

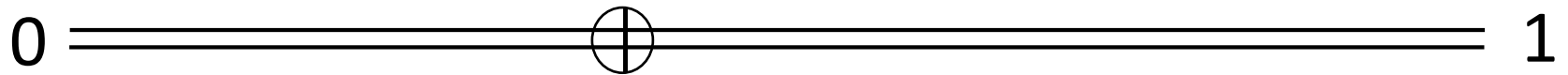


# Quantum circuits by example


- A NOT operation with classical input 0

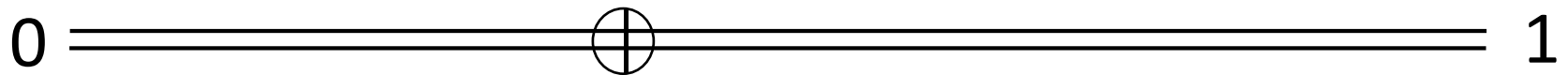

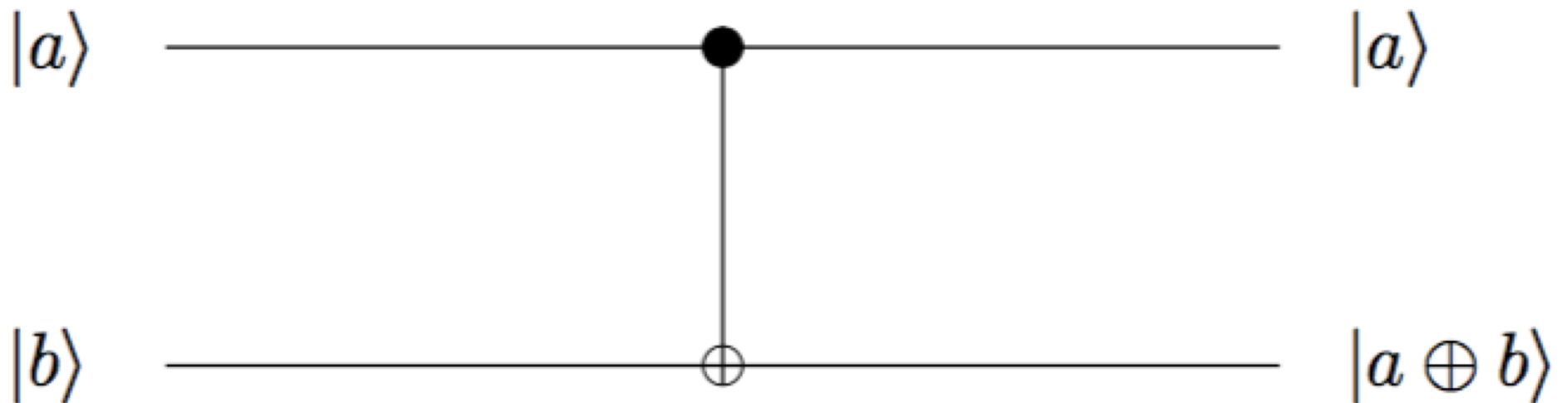- A controlled NOT operation on inputs (superpositions)  $a$ ,  $b$  with control  $a$




# Quantum circuits by example

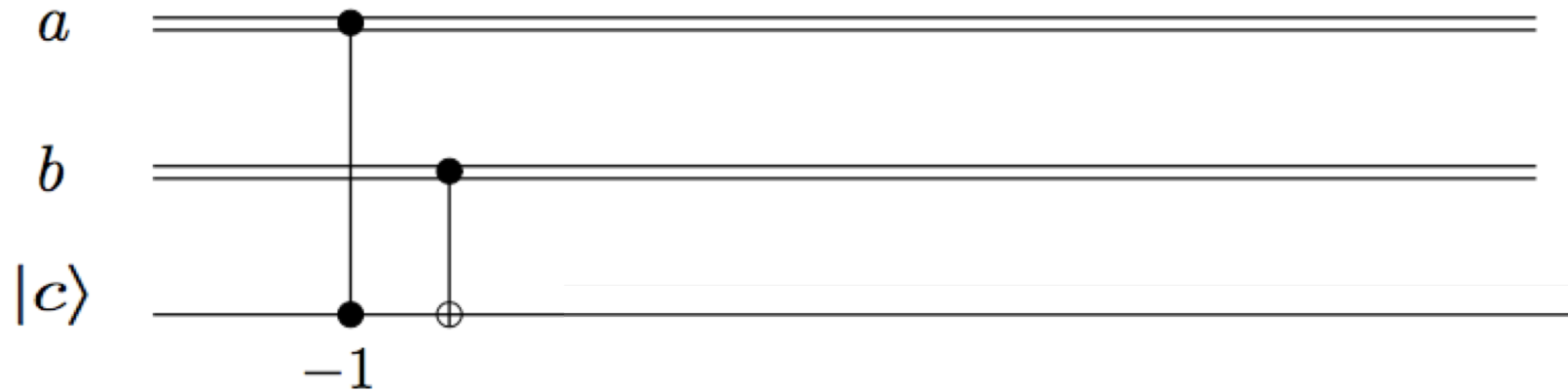



# Quantum circuits by example

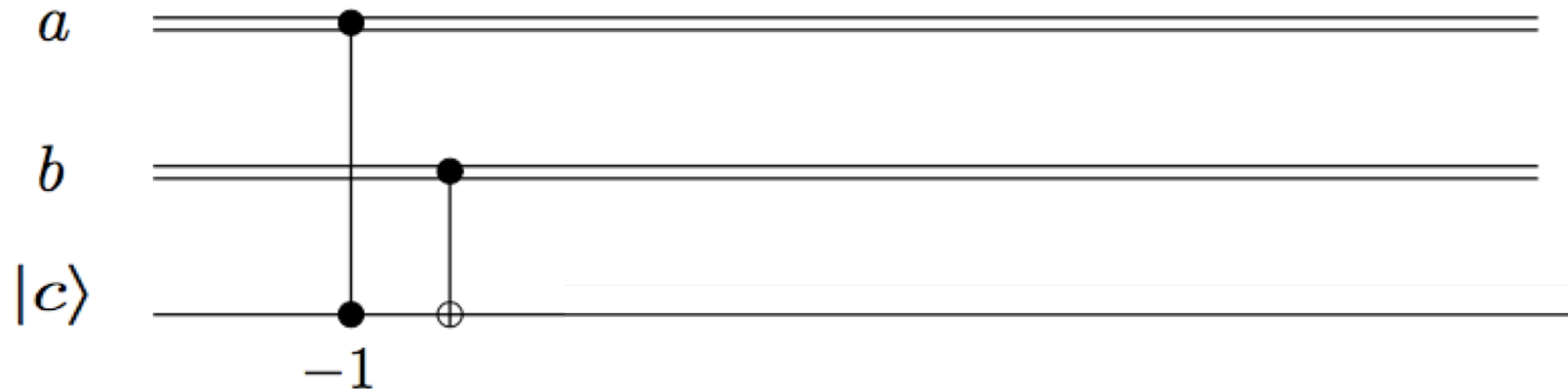


- A controlled  $\sigma_z = \begin{pmatrix} 1 & 0 \\ 0 & -1 \end{pmatrix}$  operation with control  $a$  and target  $|c\rangle$
- Then a controlled NOT operation with control  $b$  and target which is the output of the first operation
- Here  $a$  and  $b$  are classical bits


# A circuit for superdense coding

1. Alice: If  $a = 1$ , apply  $\sigma_z$  to qubit A, where
2. Alice: If  $b = 1$ , apply NOT to qubit A
3. Alice: send A to Bob
4. Bob: Apply a controlled-NOT to (A,B) (A is the control)
5. Bob: Apply a Hadamard transform to A
6. Bob: Measure A and B and output the result

# A circuit for superdense coding

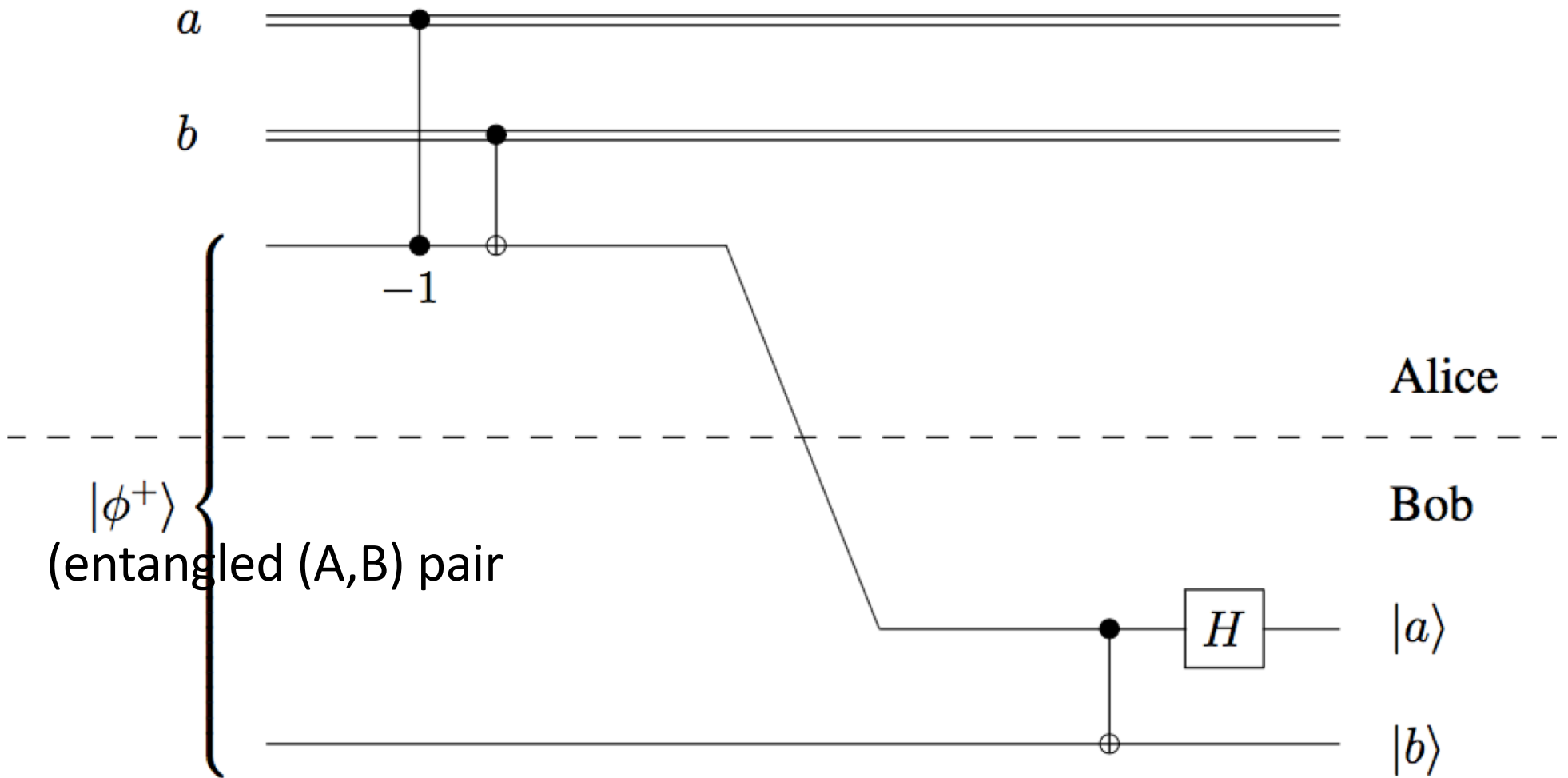


# A circuit for superdense coding

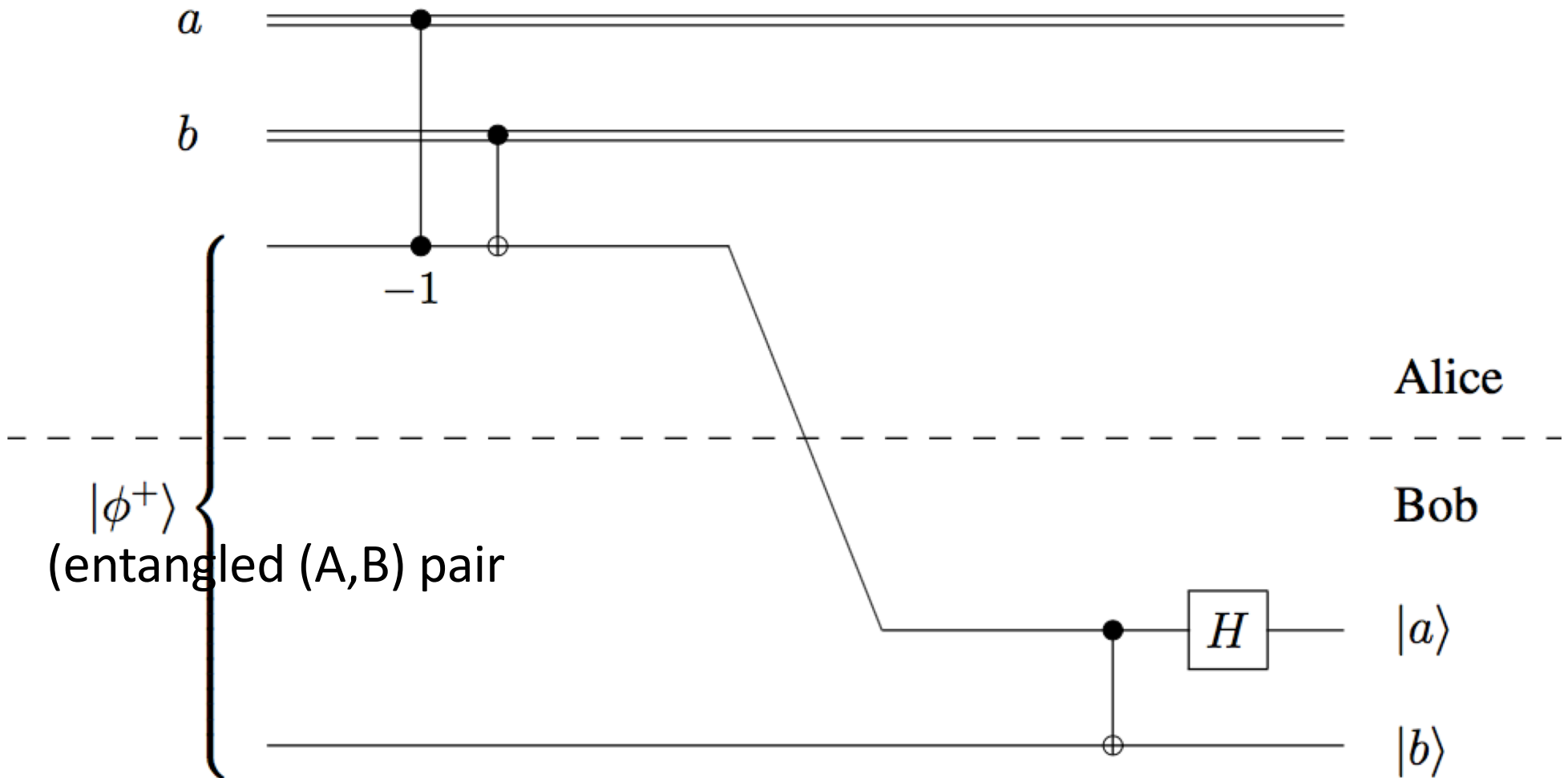

- What do we get if we apply the gates in reverse order to the output?

# A circuit with multiple gates


---

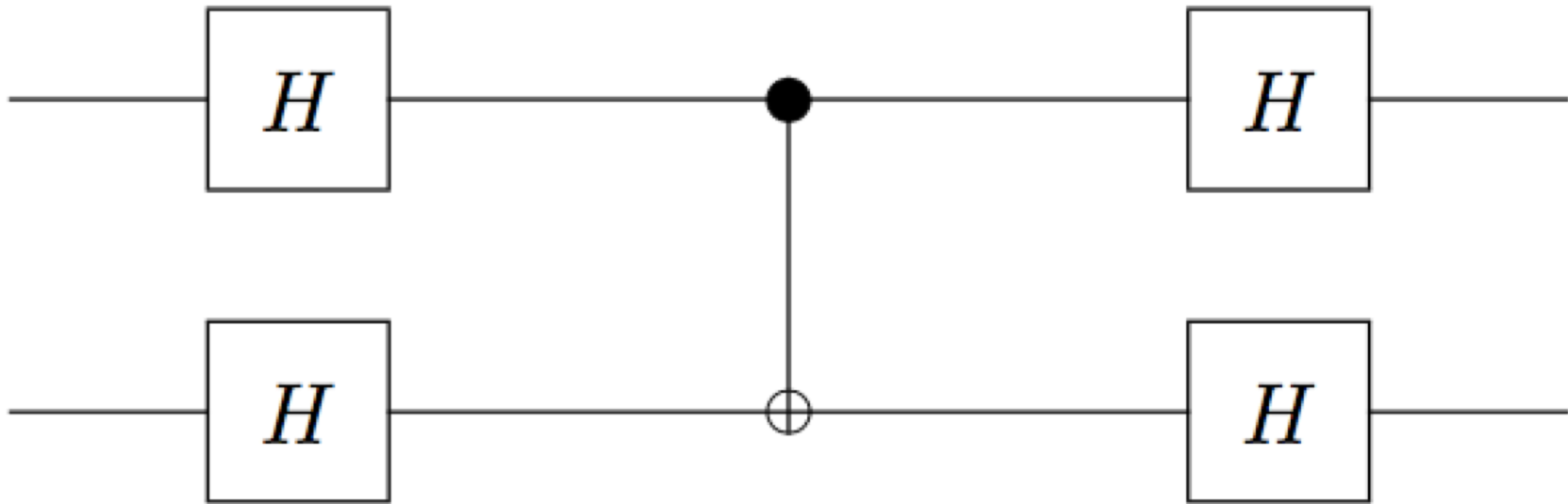

- This circuit has five gates
- Gates are evaluated from left to right
- What do you think that this circuit does?

# A circuit with multiple gates


---

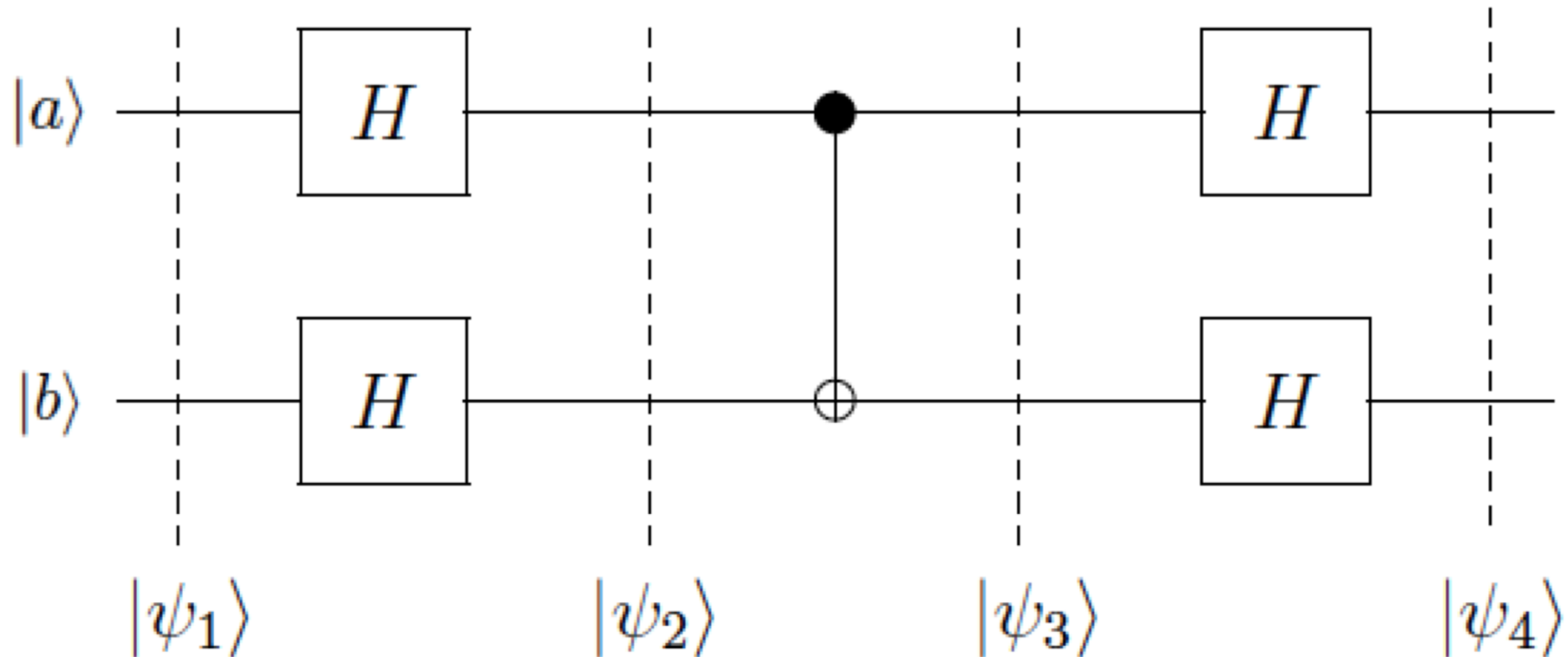

- This circuit has five gates
- Gates are evaluated from left to right
- What do you think that this circuit does?

# An equivalent circuit


---

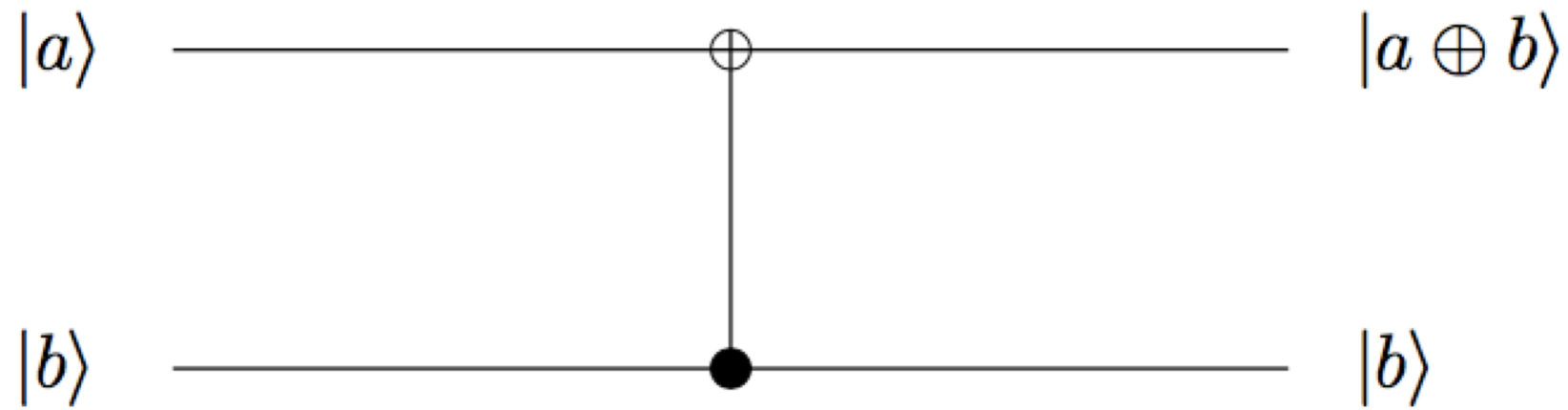
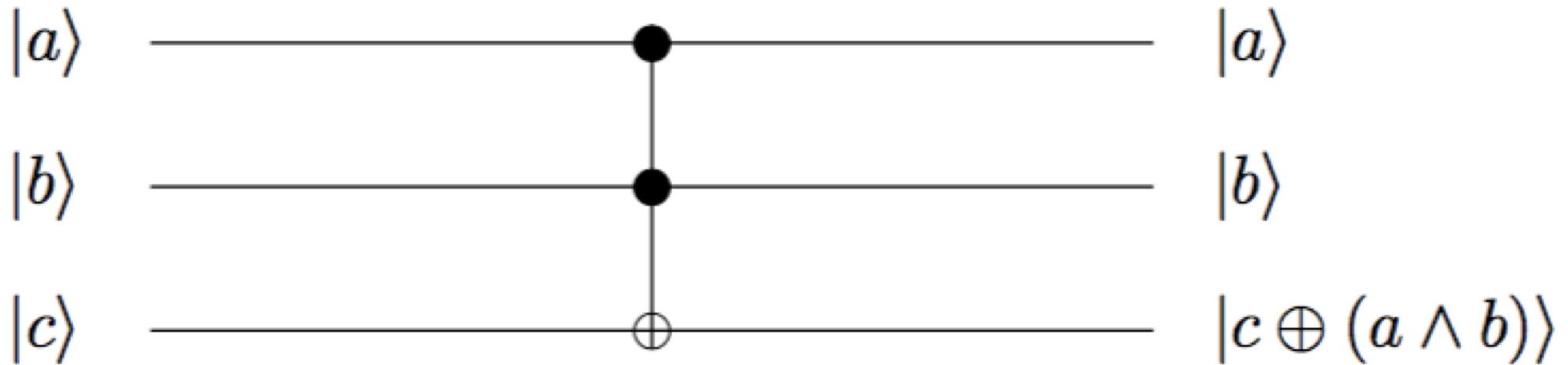
# Toffoli gates

---

- A Toffoli gate is a controlled-controlled NOT operation on inputs  $a, b, c$  in  $\{0,1\}$ ; here  $a$  and  $b$  are the controls




- If  $c = 0$ , this gate computes a AND  $b$


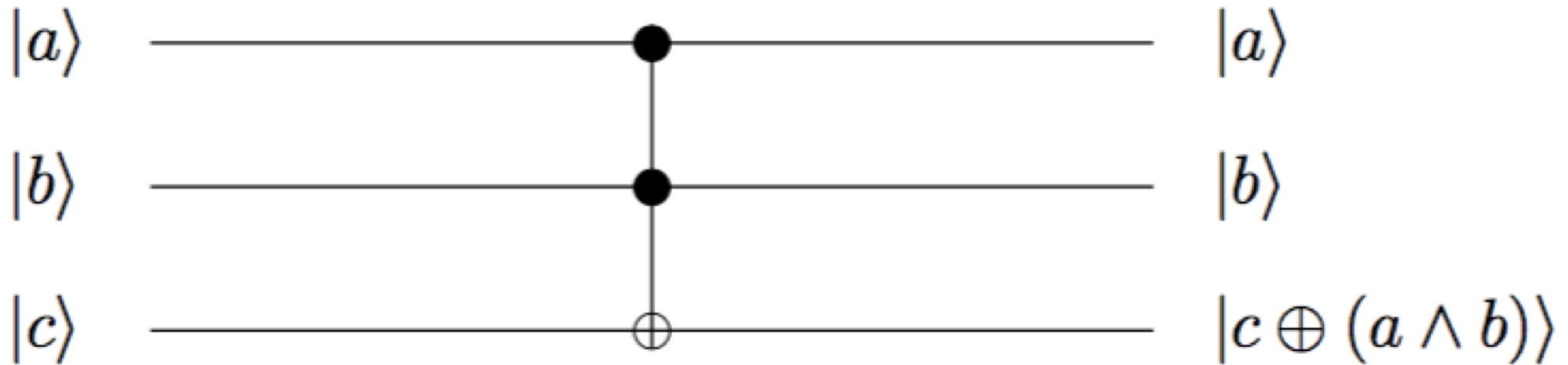
# Toffoli gates

---

- A Toffoli gate is a controlled-controlled NOT operation on inputs  $a, b, c$  in  $\{0,1\}$ ; here  $a$  and  $b$  are the controls



- What is the matrix representing this operation?

# Quantum circuit summary

---

- Qubits are represented as horizontal lines, and the number of input and output bits are equal
- Operations and measurement are represented using various symbols, and are applied from left to right

# Simulating classical circuits


---

- Can any classical circuit be simulated by a quantum circuit?

# Simulating classical circuits

---


- AND gates

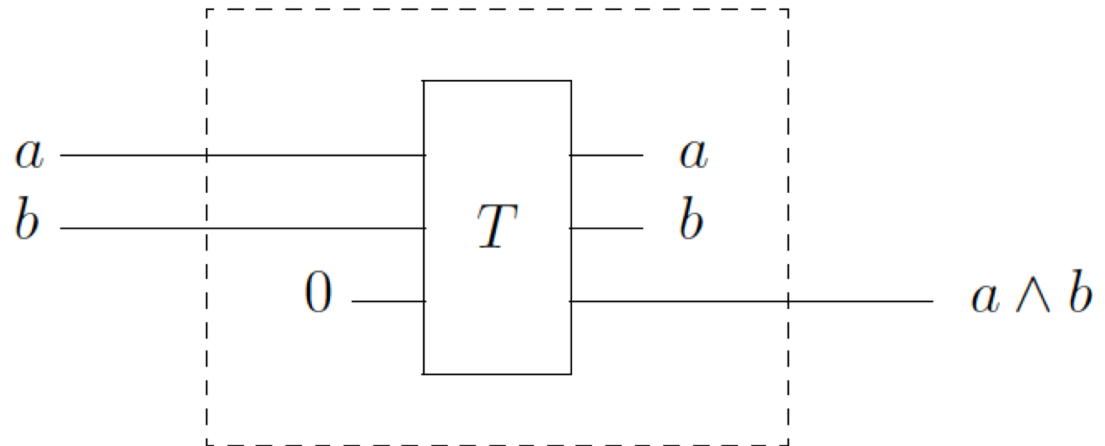

# Simulating classical circuits

---

- AND gates

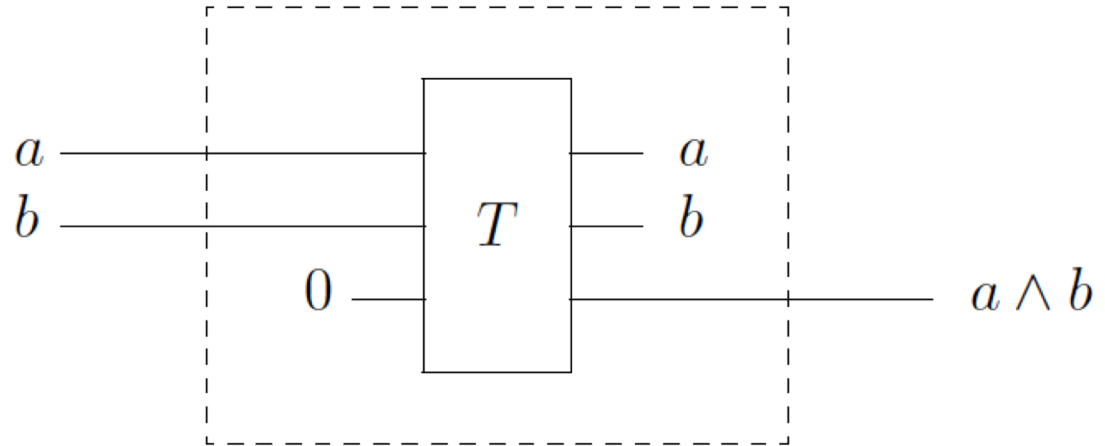


- NOT gates

# Simulating classical circuits

---

- AND gates

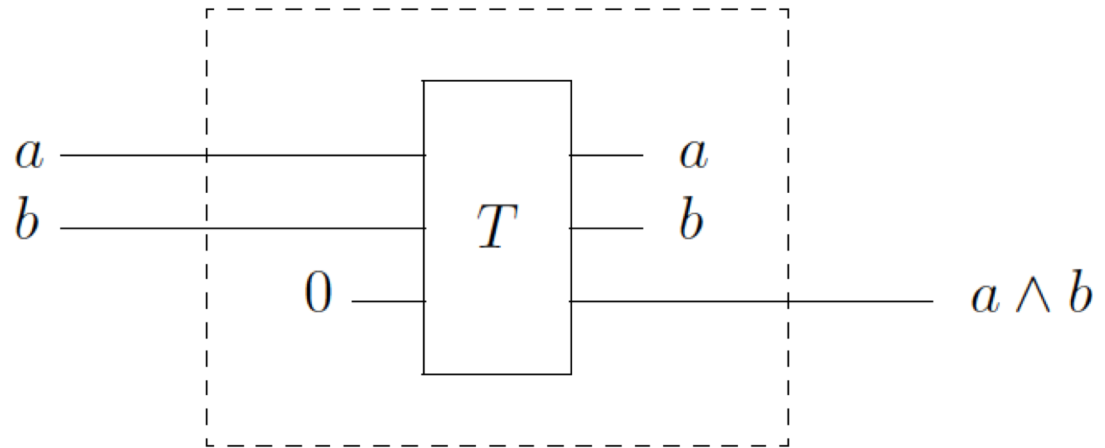


- NOT gates



# Simulating classical circuits

- AND gates

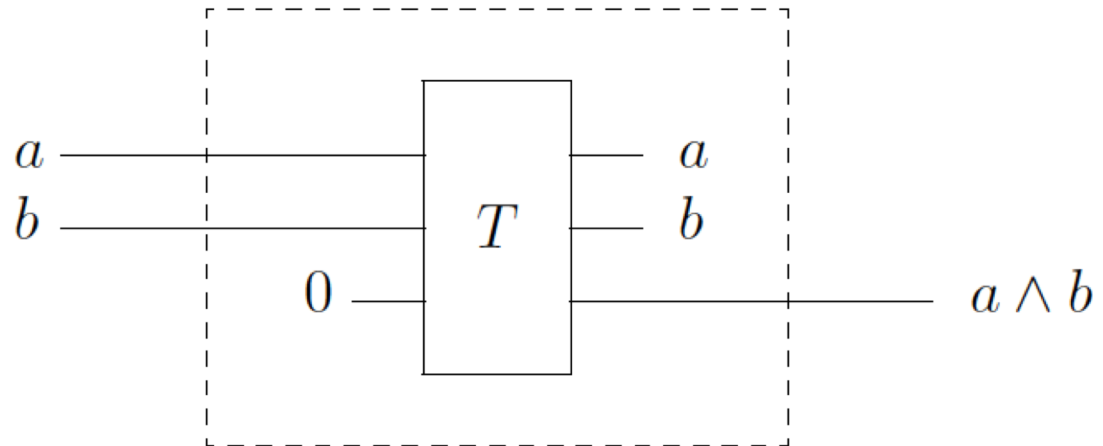

- NOT gates




- NOT can also be simulated by Toffoli – how?

# Simulating classical circuits

---

- AND gates

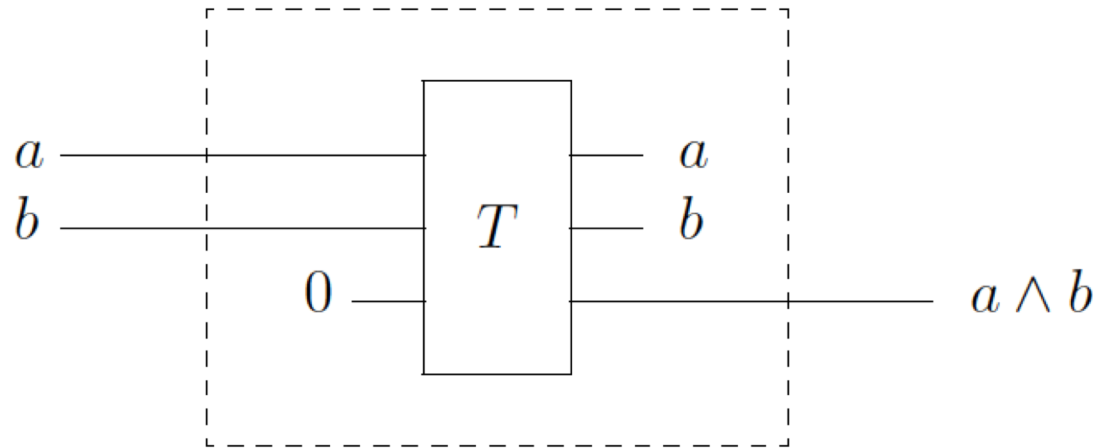

- NOT gates




- Fanout



# Simulating classical circuits

- AND gates

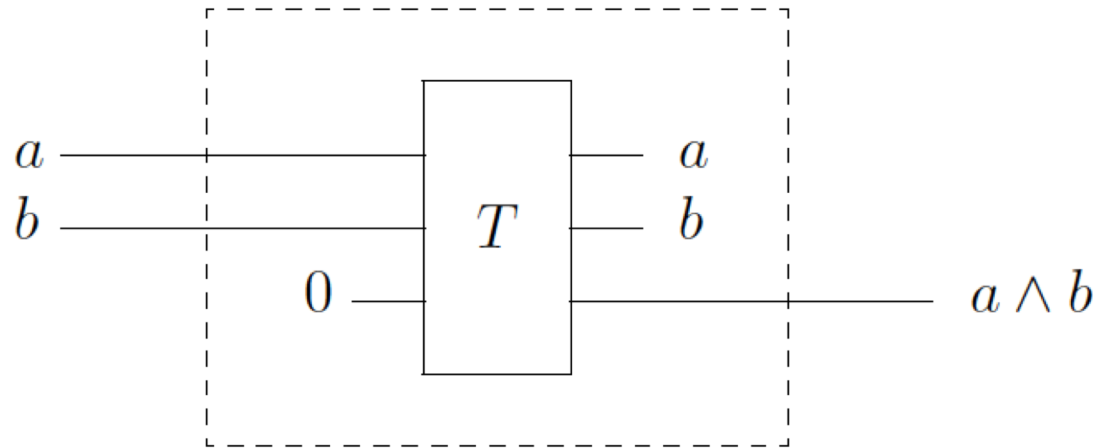

- NOT gates




- Fanout



# Simulating classical circuits


- AND gates

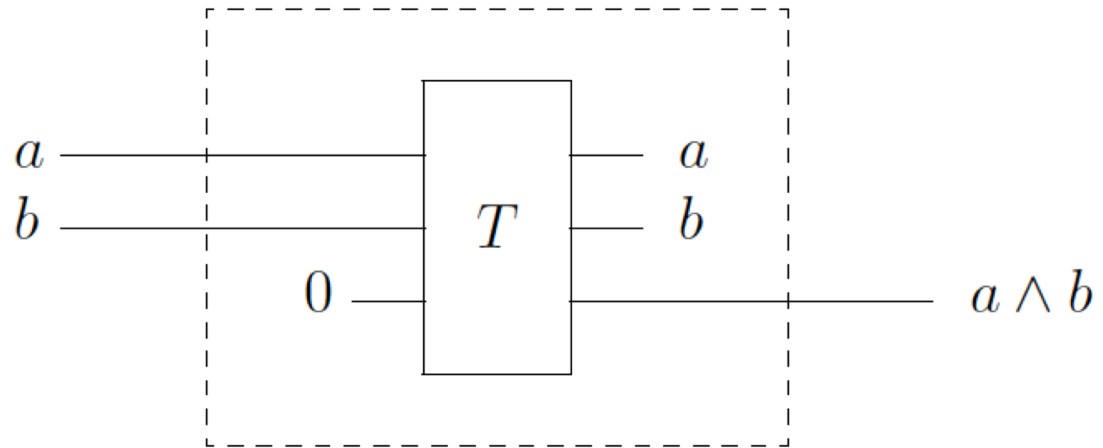

- NOT gates




- Fanout

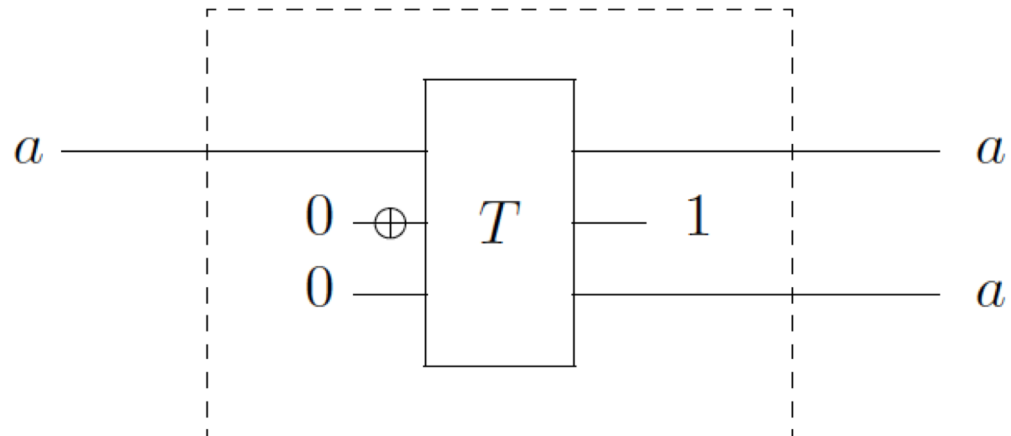

# Simulating classical circuits


- AND gates

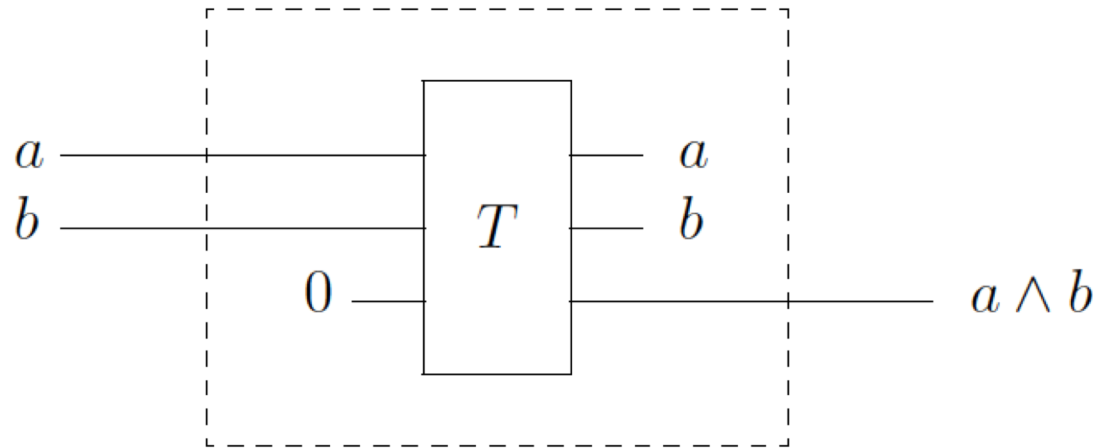

- NOT gates



- Fanout

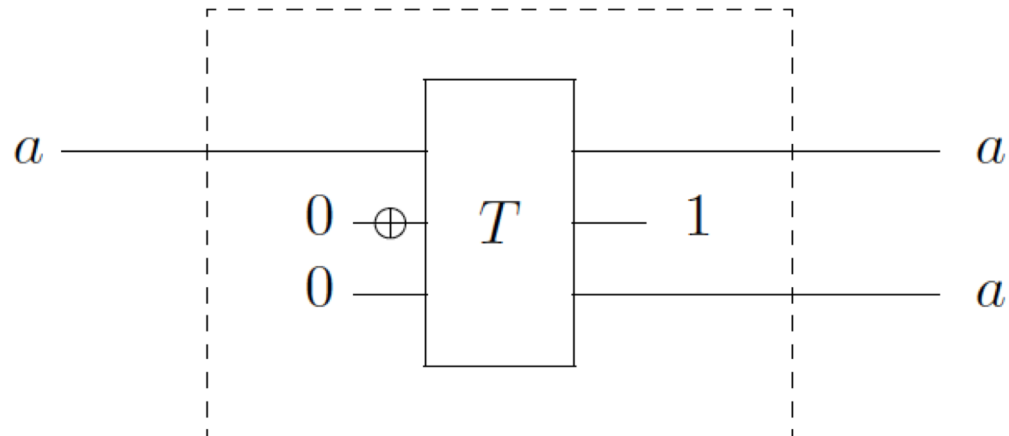


# Simulating classical circuits

---


- All of the operations needed for simulating classical circuits map classical states to classical states
- Such operations can be represented by permutation matrices
- Circuits or operations that always map classical states to classical states are called *reversible* operations or circuits

# Simulating classical circuits


---

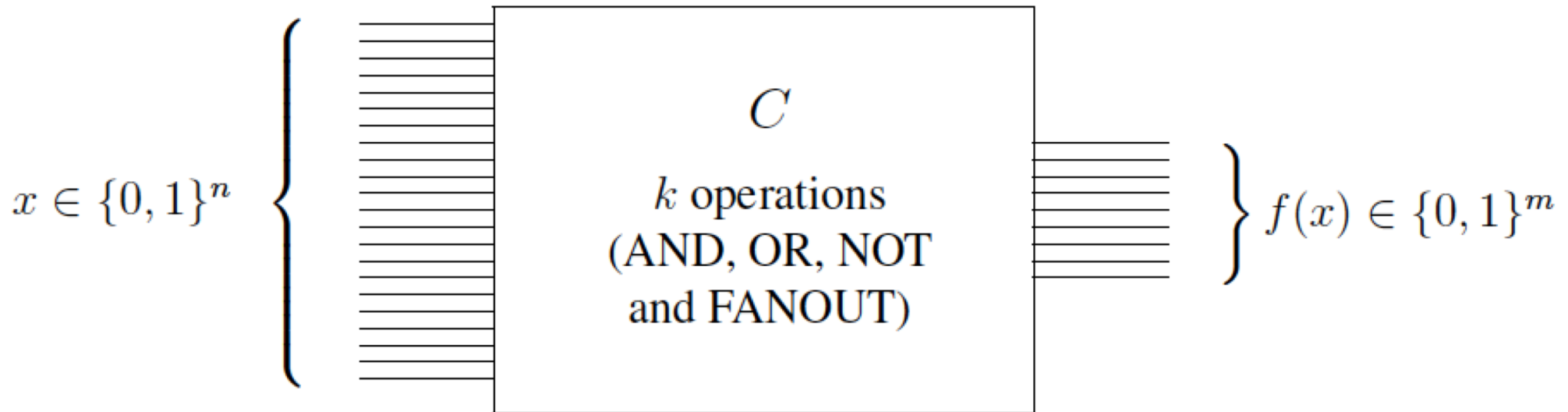


# Simulating classical circuits

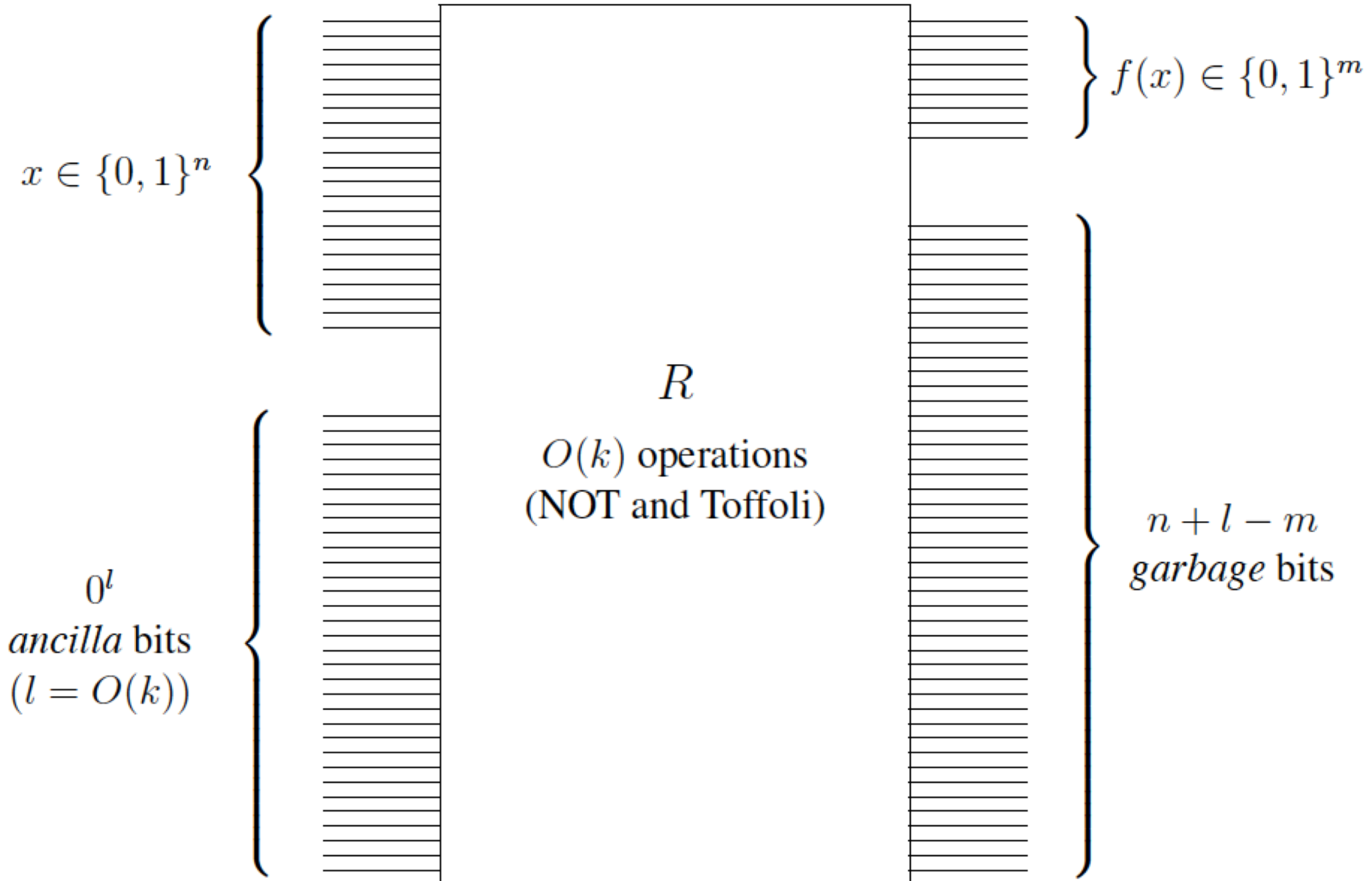

# Simulating classical circuits

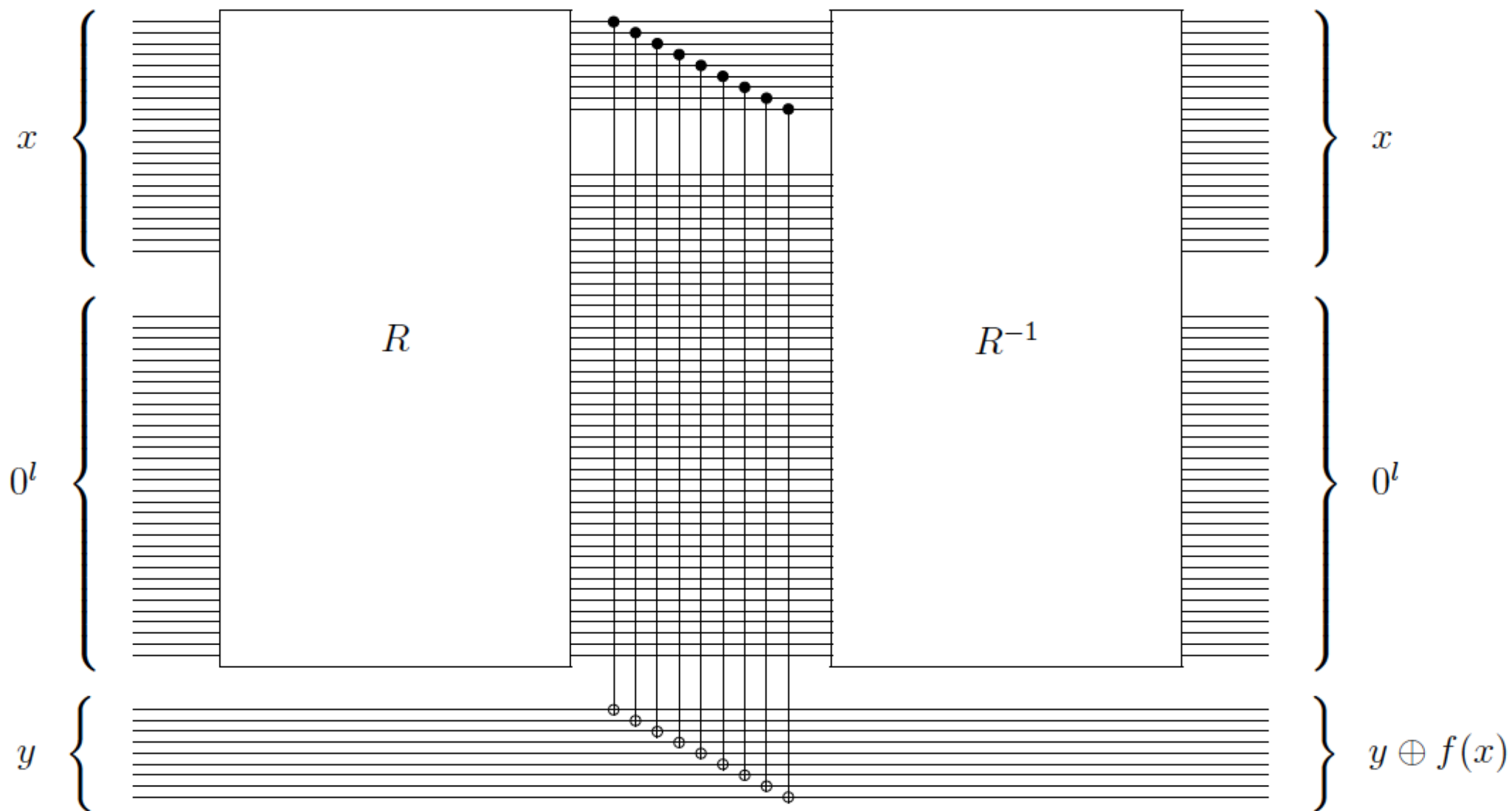


# Simulating classical circuits

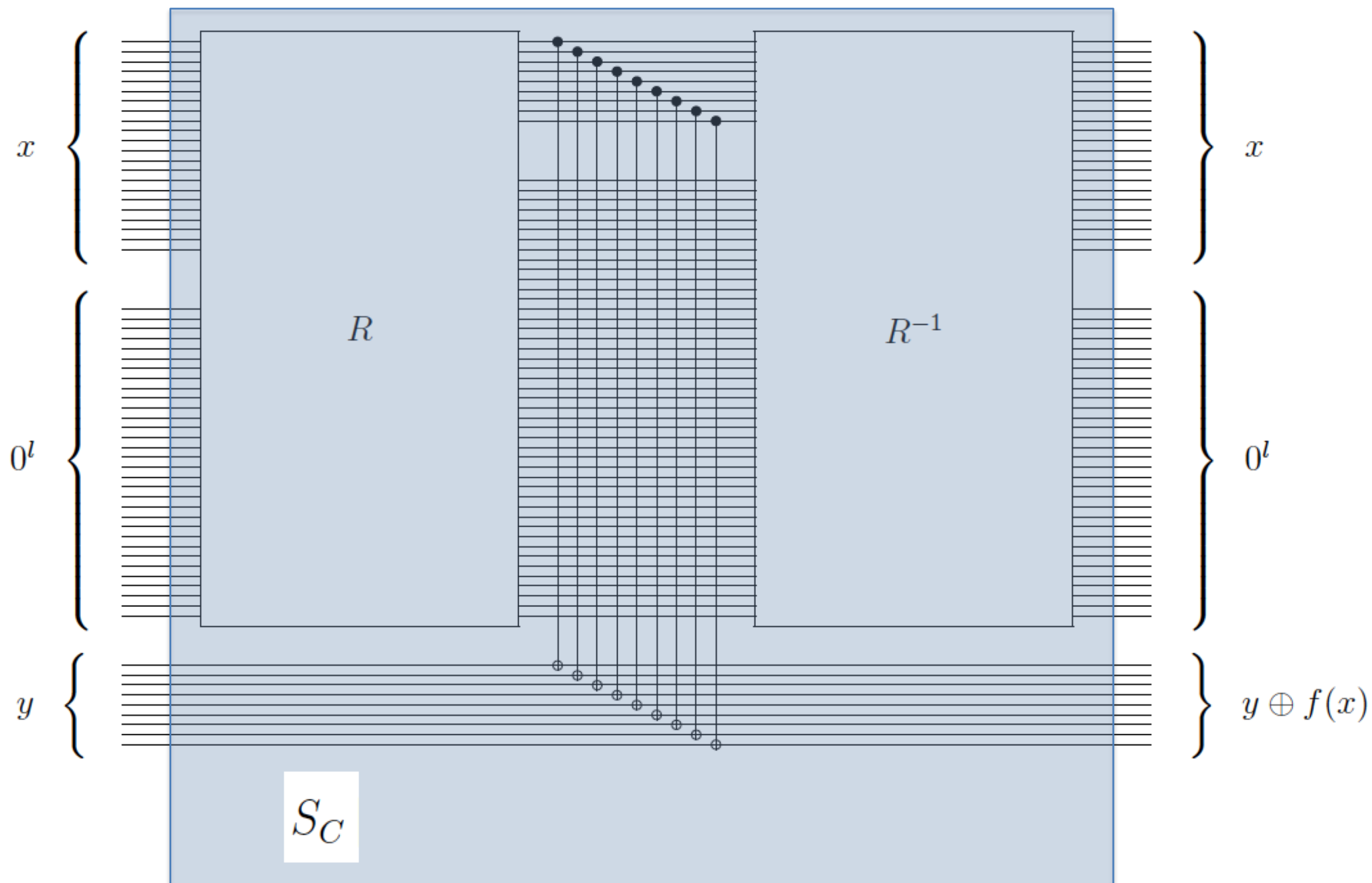



# Simulating classical circuits

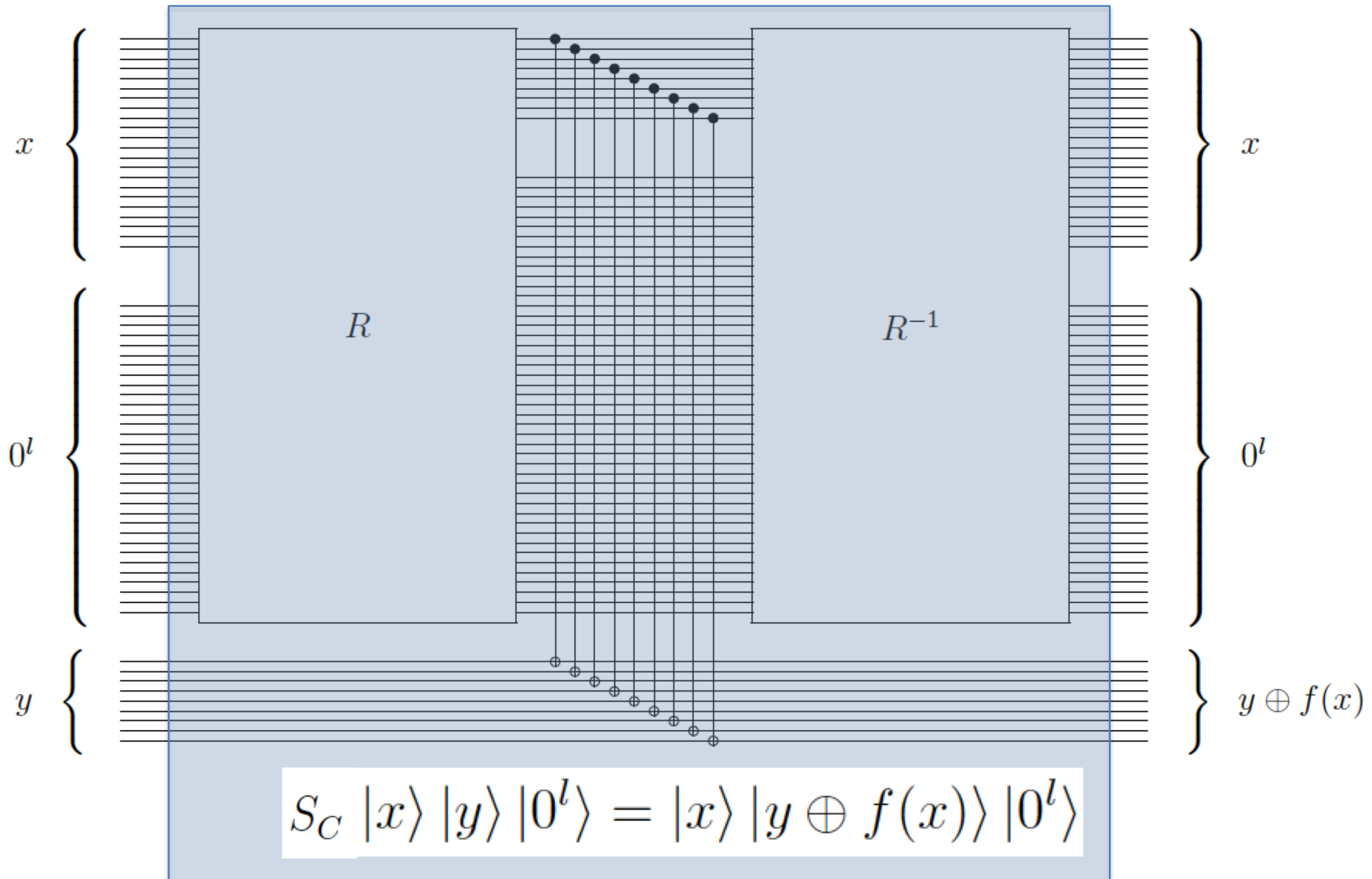

# Summary

---

- We can describe interesting protocols on quantum bits using quantum circuits, e.g. superdense coding
- Quantum circuits can efficiently simulate classical deterministic circuits if  $f: \{0,1\}^n \rightarrow \{0,1\}^m$  can be computed by classical circuit  $C$ , then our simulation procedure generates a *reversible* circuit  $S_C$  that satisfies

$$S_C |x\rangle |y\rangle |0^l\rangle = |x\rangle |y \oplus f(x)\rangle |0^l\rangle$$

# Next class

---

- Universal quantum circuits
- Quantum complexity classes