

CpSc 513: OBDD Examples

Mark Greenstreet


February 4, 2020

Outline:

- [OBDD examples: majority gates](#)
- [A simple model checking example](#)

OBDD example: majority gates

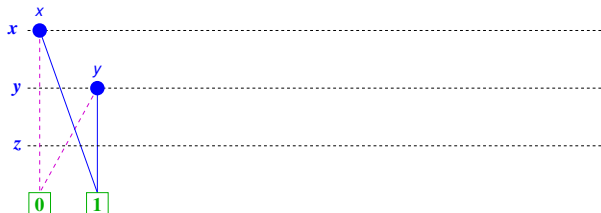
$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$



- OBDDs for x and y are simple.
- To get the OBDD for $x \wedge y$ we use Apply

OBDD example: majority gates
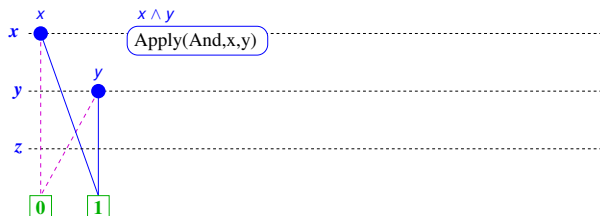
$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$



- OBDDs for x and y are simple.
- To get the OBDD for $x \wedge y$ we use Apply
 - ▶ x is first variable in the order

OBDD example: majority gates


$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$



- OBDDs for x and y are simple.
- To get the OBDD for $x \wedge y$ we use Apply
 - ▶ x is first variable in the order
 - ▶ false branch at x for $\text{Apply}(\text{AND}, x, y)$ is $\text{Apply}(\text{And}_{x \leftarrow 0}, y|_{x \leftarrow 0})$ which simplifies to $\text{Apply}(\text{And}, 0, y)$. Likewise, the true branch is $\text{Apply}(\text{And}, 1, y)$.
 - ▶ $\text{Apply}(\text{And}, 0, y)$ simplifies to 0 , and $\text{Apply}(\text{And}, 1, y)$ simplifies to y .

OBDD example: majority gates

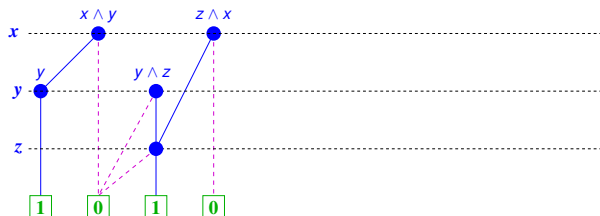
$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$



- OBDDs for x and y are simple.
- To get the OBDD for $x \wedge y$ we use Apply
- The OBDDs for $y \wedge z$ and $z \wedge x$ are similar.
- To avoid lots of crossing edges; I'll use multiple **0** and **1** leaves. To keep the OBDD canonical, all **0** leaves are actually the same node, and likewise for the **1** leaves.

OBDD example: majority gates

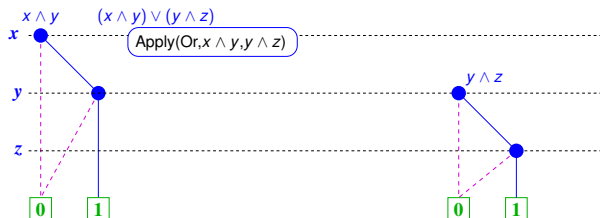
$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$



- Use apply to get OBDD for $(x \wedge y) \vee (y \wedge z)$.

OBDD example: majority gates

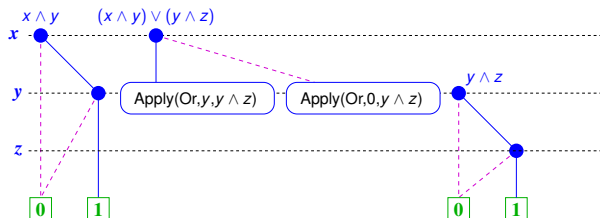
$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$



- Use apply to get OBDD for $(x \wedge y) \vee (y \wedge z)$.
 - ▶ $((x \wedge y) \vee (y \wedge z))|_{x \leftarrow 0} = 0 \vee (y \wedge z)$,
 - ▶ $((x \wedge y) \vee (y \wedge z))|_{x \leftarrow 1} = y \vee (y \wedge z)$.

OBDD example: majority gates

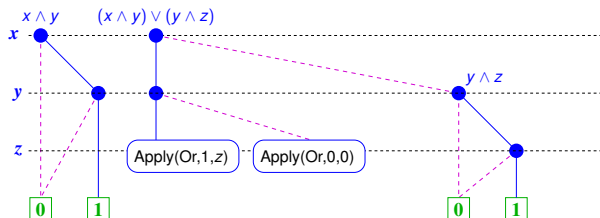
$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$



- Use apply to get OBDD for $(x \wedge y) \vee (y \wedge z)$.
 - ▶ $((x \wedge y) \vee (y \wedge z))|_{x \leftarrow 0} = 0 \vee (y \wedge z)$,
 $((x \wedge y) \vee (y \wedge z))|_{x \leftarrow 1} = y \vee (y \wedge z)$.
 - ▶ $0 \vee (y \wedge z) = y \wedge z$,
 $(y \vee (y \wedge z))|_{y \leftarrow 0} = 0 \vee (0 \wedge z) = 0$,
 $(y \vee (y \wedge z))|_{y \leftarrow 1} = 1 \vee (1 \wedge z) = 1$.

OBDD example: majority gates

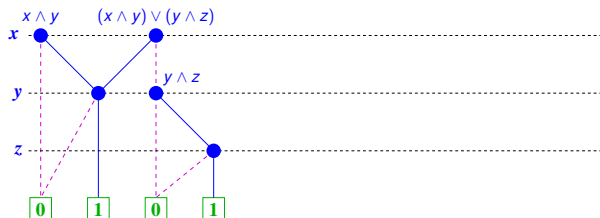
$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$



- Use apply to get OBDD for $(x \wedge y) \vee (y \wedge z)$.
 - ▶ $((x \wedge y) \vee (y \wedge z))|_{x \leftarrow 0} = 0 \vee (y \wedge z)$,
 $((x \wedge y) \vee (y \wedge z))|_{x \leftarrow 1} = y \vee (y \wedge z)$.
 - ▶ $0 \vee (y \wedge z) = y \wedge z$,
 $(y \vee (y \wedge z))|_{y \leftarrow 0} = 0 \vee (0 \wedge z) = 0$,
 $(y \vee (y \wedge z))|_{y \leftarrow 1} = 1 \vee (1 \wedge z) = 1$.
 - ▶ $\therefore ((x \wedge y) \vee (y \wedge z))|_{x \leftarrow 1} = y \vee (y \wedge z) = y$

OBDD example: majority gates

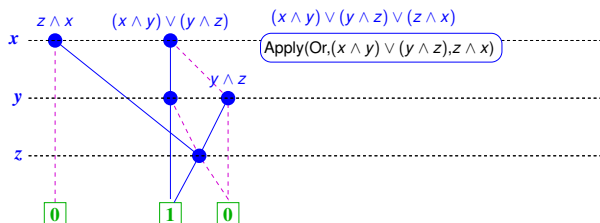
$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$



- Use apply to get OBDD for $(x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$.

OBDD example: majority gates

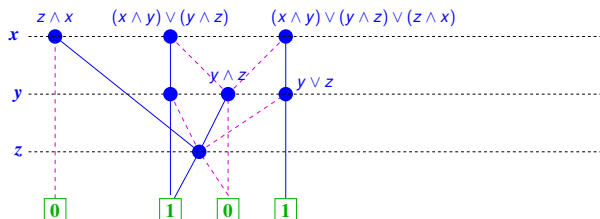
$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$



- Use apply to get OBDD for $(x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$.

OBDD example: majority gates

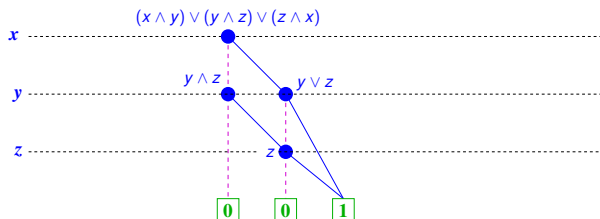
$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$



- I'll reduced the clutter and only showed the subgraph for $(x \wedge y) \vee (y \wedge z)$.

OBDD example: majority gate – the product-of-sums version
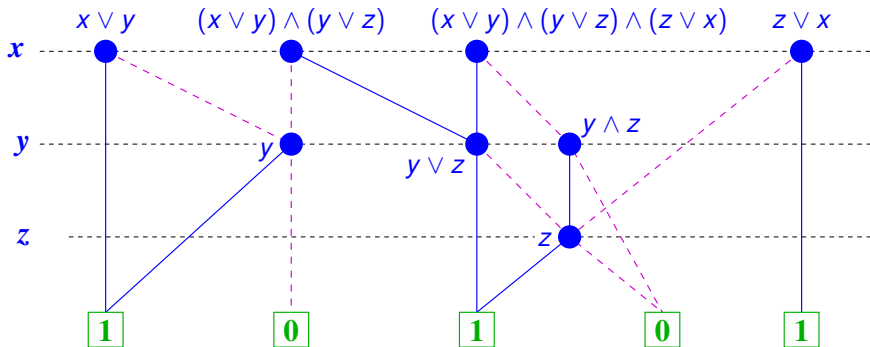
$$\text{maj2}(x, y, z) = (x \vee y) \wedge (y \vee z) \wedge (z \vee x)$$



OBDD example: majority gates – are they the same?

$$\text{maj1}(x, y, z) = (x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$


$$\text{maj2}(x, y, z) = (x \vee y) \wedge (y \vee z) \wedge (z \vee x)$$

$$(x \wedge y) \vee (y \wedge z) \vee (z \wedge x)$$

x

y

z

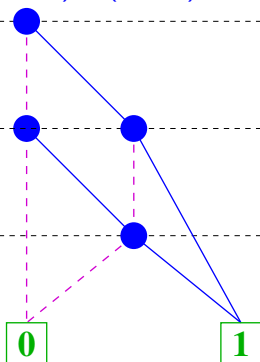


$$(x \vee y) \wedge (y \vee z) \wedge (z \vee x)$$


x

y

z

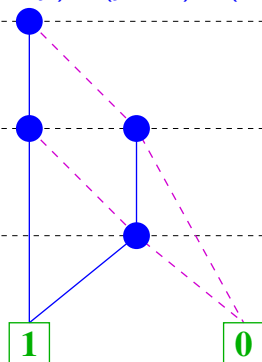


Now I C

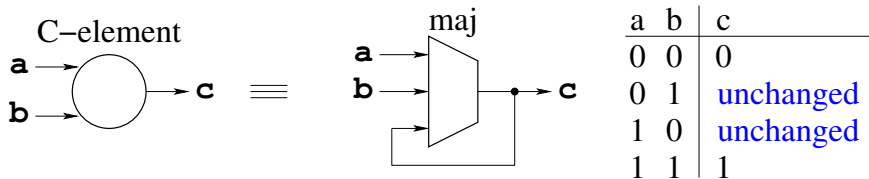

- A C-element is a state-holding circuit – kind of like a flip-flop
- The value of c is the value that a and b had the last time they agreed.
- Originally described in:
D.E. Muller and W.S. Bartky, “A Theory of Asynchronous Circuits”,
Proceedings of the International Symposium on Switching Theory,
pp. 204–243, 1959.

Fun with C-elements

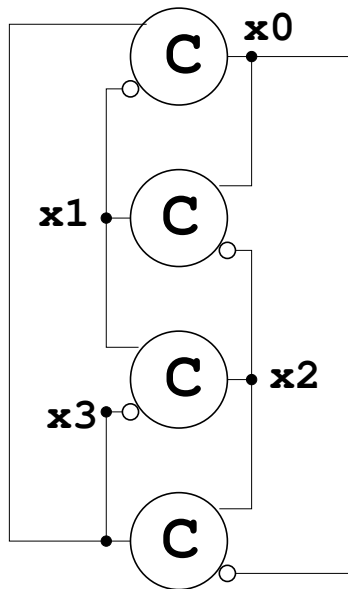

Temporal Logic

- LTL: Linear time logic: properties that hold for **all** traces
 - ▶ p : The property p holds in the current state.
 - ▶ $\Box p$: **Always** – the property p holds in this state and all subsequent states.
 - ▶ $\Diamond p$: **Eventually** – The property p in this state or some future state.
 - ▶ Example: $\Box(req \rightarrow \Diamond ack)$ – From all states in which req holds, ack will eventually hold.
- CTL: Computational Tree Logic – traces are viewed as branching trees of all possible behaviours.