

# Determining the Existence of DC Operating Points in Circuits

Mohamed Zaki  
Department of Computer Science,  
University of British Columbia

Joint work with Ian Mitchell and Mark Greenstreet

---

Nov 23<sup>nd</sup>, 2009




# Talk Outline


- ❑ Introduction
- ❑ Formal Verification of Circuits: An Overview
- ❑ DC Analysis:
  - ❑ Basic Concepts
  - ❑ A Formal Approach
- ❑ Case Studies
- ❑ Enhancing the Verification with invariants
- ❑ Discussion

# Hybrid Systems


## Transportation Systems

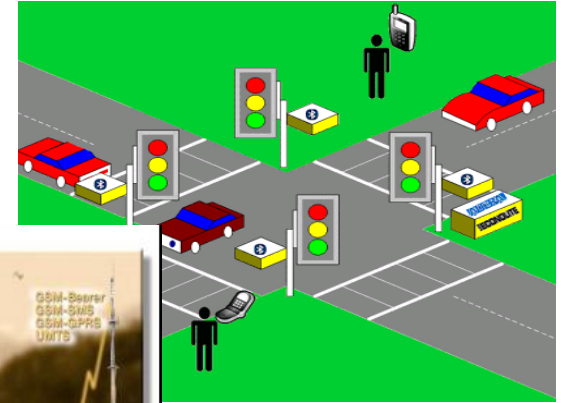


Vehicle:  
Mechanical + Computer System

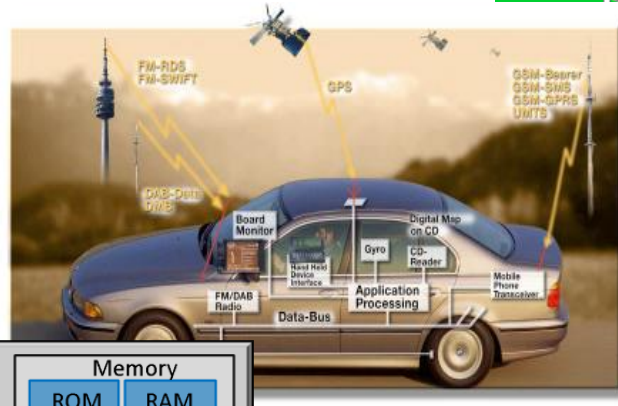

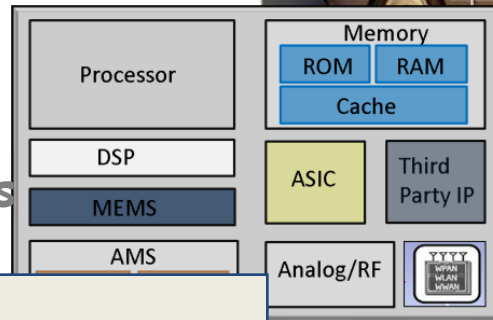Computer System  
Digital and AMS designs



Digital Design

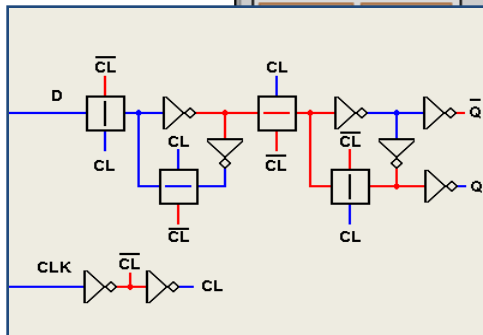

<http://www.eecs.berkeley.edu/~apinto/esd>


<http://www.cs.unc.edu/~templar/>

<http://nortonkit.net/>

 
# CMOS Design: An introduction

CMOS: **Complementary metal–oxide–semiconductor**

Building blocks of integrated circuits and microprocessors



**Example**

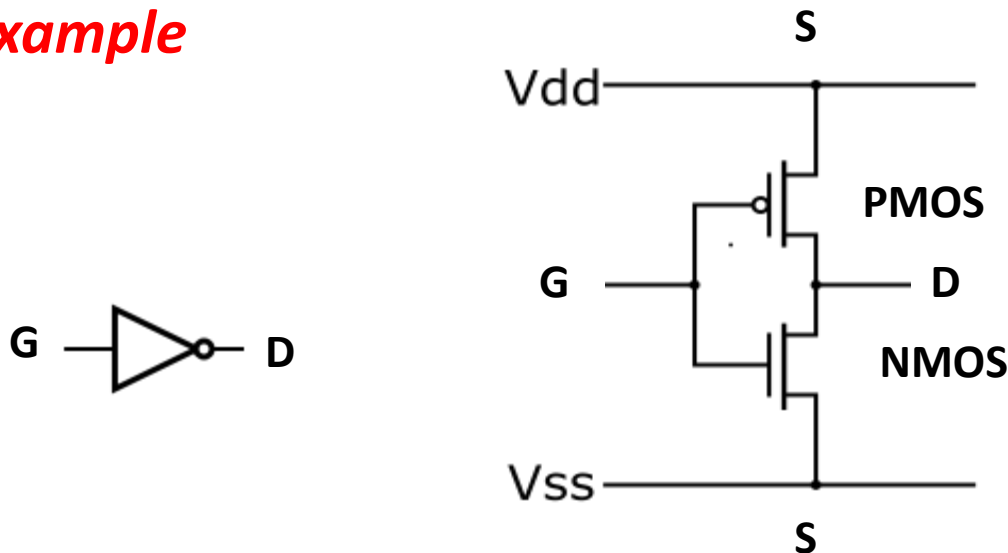

# Circuits Verification

- Transistor level models
- Circuit simulator (Spice)
  - Steady State simulation
  - AC simulation
  - Transient simulation
  - Parameter sweeping
  - Statistical variation (Monte Carlo)

# *DC operating point*



*To which voltages will the nodes of the circuit settle if the inputs to the circuit remain indefinitely at their fixed values?*

## Some Applications

- Identify qualitative characteristics of a circuit (e.g., existence of stable behavior)
- Determine initial conditions prior to transient analysis
- Determine linearization point prior to ac small signal analysis

  
# Ring Oscillators: A Motivating Example

- **Ring oscillators** are a common component used in a variety of analog applications
- Uses an **odd** number of **inverter** stages to produce **oscillating** “0” and “1” signals




- Can we generate quadrature signals using ring oscillators?

# Rambus Oscillators


 




# Rambus Oscillators

 

# Rambus Oscillators

  


Circuits Parameters are guessed

# Rambus Oscillators


*r*: ring inverter

*b*: bridge inverter

Width Ratio =  $W_r/W_b \gg 1$

 

Width Ratio =  $W_r/W_b \ll 1$

 

*For some ratios, there are some initial conditions that lead to oscillation, while others lead to stable behavior. GLSVLSI'08*

- Digital abstraction doesn't hold
- Functionality is sensitive to the exact sizing
- Sensitivities to initial conditions for some sizes

# An Example from the "Real world"

- The example is extracted from an actual design failure
  - Some issues were only found in measurement of **fabricated** test chips
  - The design was **validated** as well as any analog designs are in practice today


## Challenges for Verification

*For a given choice of transistor sizes, show that the circuit operates properly for<sup>v</sup> all initial conditions almost*


# Talk Outline

- ❑ Introduction
- ❑ Formal Verification of Circuits: An Overview
- ❑ DC Analysis:
  - ❑ Basic Concepts
  - ❑ A Formal Approach
- ❑ Case Studies
- ❑ Enhancing the Verification with invariants
- ❑ Discussion


# Circuits Modelling Views

 

**Real world view**

 

**Analog world view**

 

**Digital world view**

# Challenges in Analog Verification


- Infinite **continuous** state space
  - Cannot do exhaustive **simulation** of individual traces/trajectories
- Strong continuous **nonlinear** behavior
  - No closed form solution for **differential equations**
  - Numerical methods have **inaccuracies**
- Properties are hard to specify

# Formal Verification

- Use mathematical reasoning to prove **correctness**
- **Exploration** of all the possible behaviors
- Assures implementation **matches** specification
  - If correct, all behaviors are verified
  - If incorrect a counter-example (proof) is presented
- Verification is undecidable
  - Indeterminate results



# Research Framework

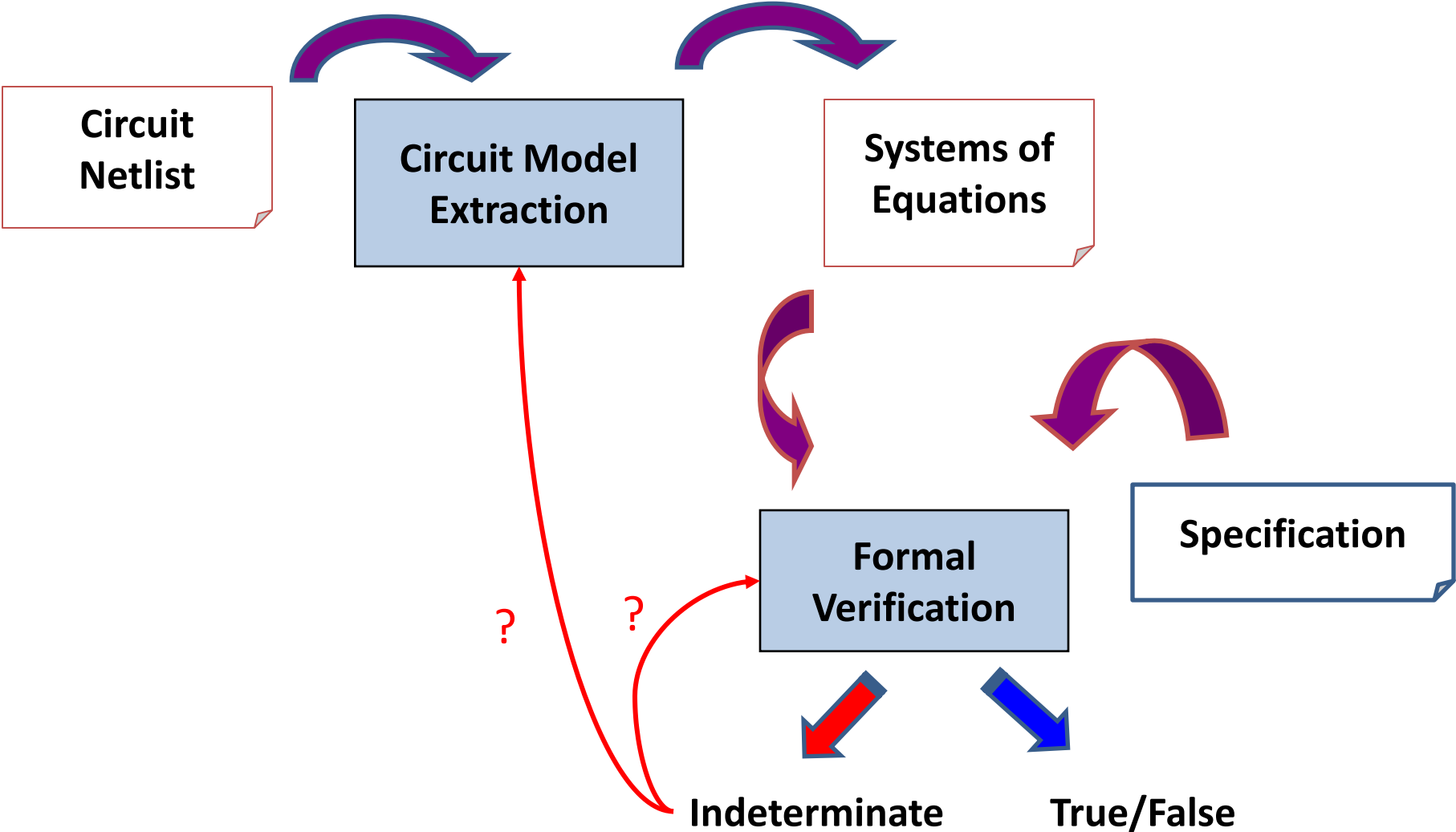

# Formal Verification of Analog Circuits

Kurshan '91, Hartong'02,

- State space decomposition, use numerical methods to build transitions


Greenstreet '98, 07, Gupta'04,  
Dang'04, Frehse'06, Little'04' 06

- Forward Reachability:  
Geometrical enclosure of  
the behavior


Freibothe'06, Walter'07,  
Tiwari'09, Denman'09

- Constraints based Verification: Decision  
procedured (e.g., SMT) Linearization of the  
behavior

(Kurshan'92)

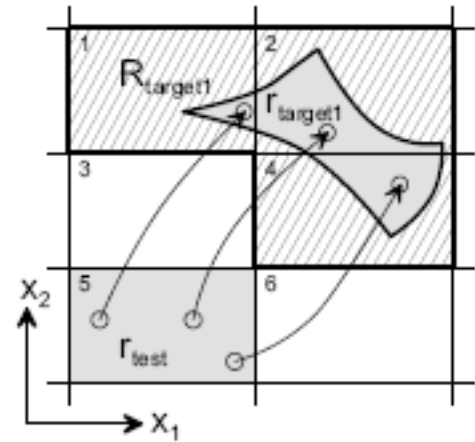

(Gupta'04)

 

# Talk Outline

- ❑ Introduction
- ❑ Formal Verification of Circuits: An Overview
- ❑ DC Analysis:
  - ❑ Basic Concepts
  - ❑ A Formal Approach
- ❑ Case Studies
- ❑ Enhancing the Verification with invariants
- ❑ Discussion

# DC Analysis

*DC operating point: To which voltages will the nodes of the circuit settle to if the inputs to the circuit remain indefinitely at their fixed values?*

Is it a requirement to have a DC operating point?

How many DC operating points does the circuit have?

Latch	Schmitt Trigger	Oscillator
2 DC OP	1 or 2 DC OP	0 DC OP

# DC Equilibrium

Given an ODE system

$$\frac{d}{dt}x = f(x, in)$$


Necessary condition for existence of DC operating point

Chosen input


$$f(x, \underline{in}) = \mathbf{0}$$

*What is the nature of the DC equilibrium points?*


Stable Equilibrium:  
DC Operating point

 

Unstable Equilibrium

 

Metastable Equilibrium

 

# Classifying DC equilibrium

Behavior of trajectories in the neighborhood of an equilibrium point is governed by the eigenvalues of the Jacobian matrix

J is Jacobian  
Matrix

Chosen input


$$J_{i,j}(f, \underline{x}, \underline{in}) = \left. \frac{\partial}{\partial x_j} f_i(x, \underline{in}) \right|_{x=\underline{x}}$$

- If all **eigenvalues** have **real** parts that are **less than zero**, then  $\underline{x}$  is a stable equilibrium point  $\Rightarrow$  DC operating point
- If any **eigenvalue** has a **positive real** part, then we will call  $\underline{x}$  an unstable equilibrium  $\Rightarrow$  no DC operating point

# Issues in locating DC Operating points

- Finding a solution to the equations of a circuit involves finding the **root** of a system of non-linear equations
- Symbolic and numerical methods **might fail** to locate all possible solutions and be guaranteed to find a solution.
- If DC equilibriums are approximately identified, how to analyze their **stability**?


# Proposed Approach

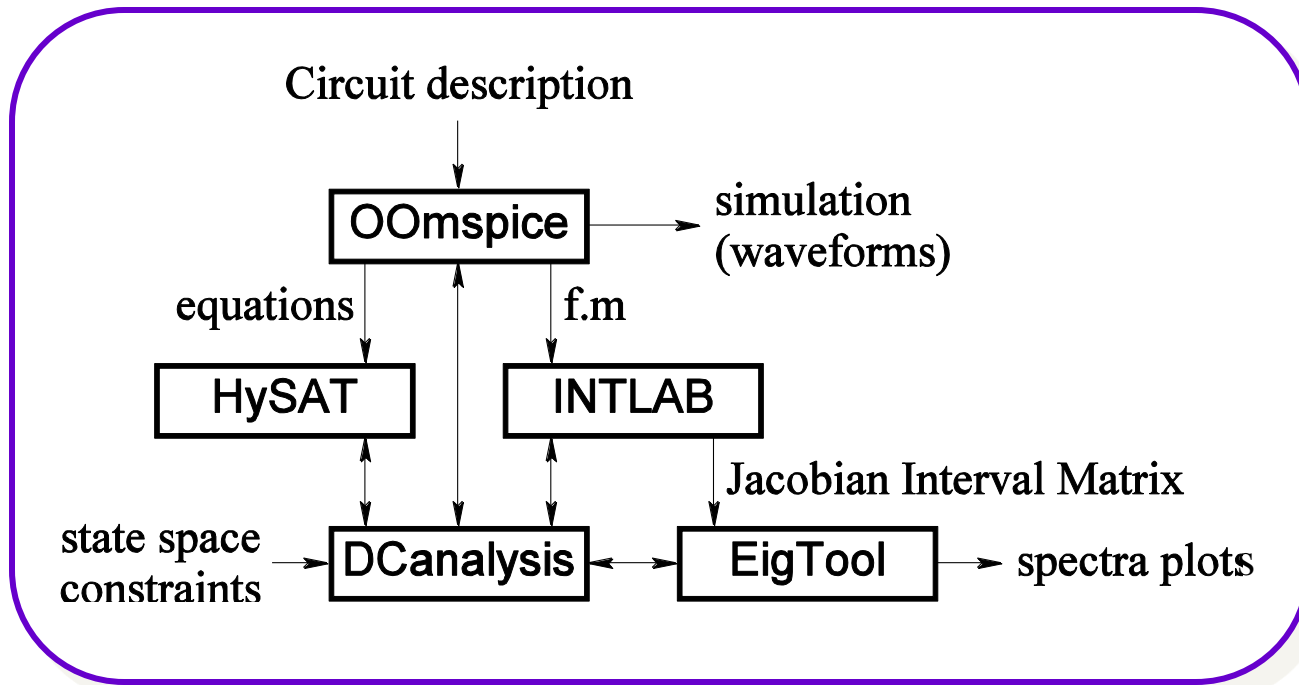

- Procedure that uses symbolic models generated from a netlist to rigorously **locate** and **classify** all of the **equilibrium points**
- Determines the existence, location and number of **DC OP**
- Implemented with a collection of public tools within **MATLAB** environment




# Proposed Approach

 


- **OOMSPICE: Object Oriented Matlab Spice**
- Circuit modeling and analysis for formal verification
- Accommodates the creation of **hierarchical** designs
- Possible addition of new electrical components and alternative **abstractions** descriptions of existing components.

# Proposed Approach

 


- Coordinates the verification tasks and uses OOm Spice to generate the circuit equations as desired by the verification tools:
- **DC equations** for Hysat
- **ODE system** for INTLAB

# Proposed Approach

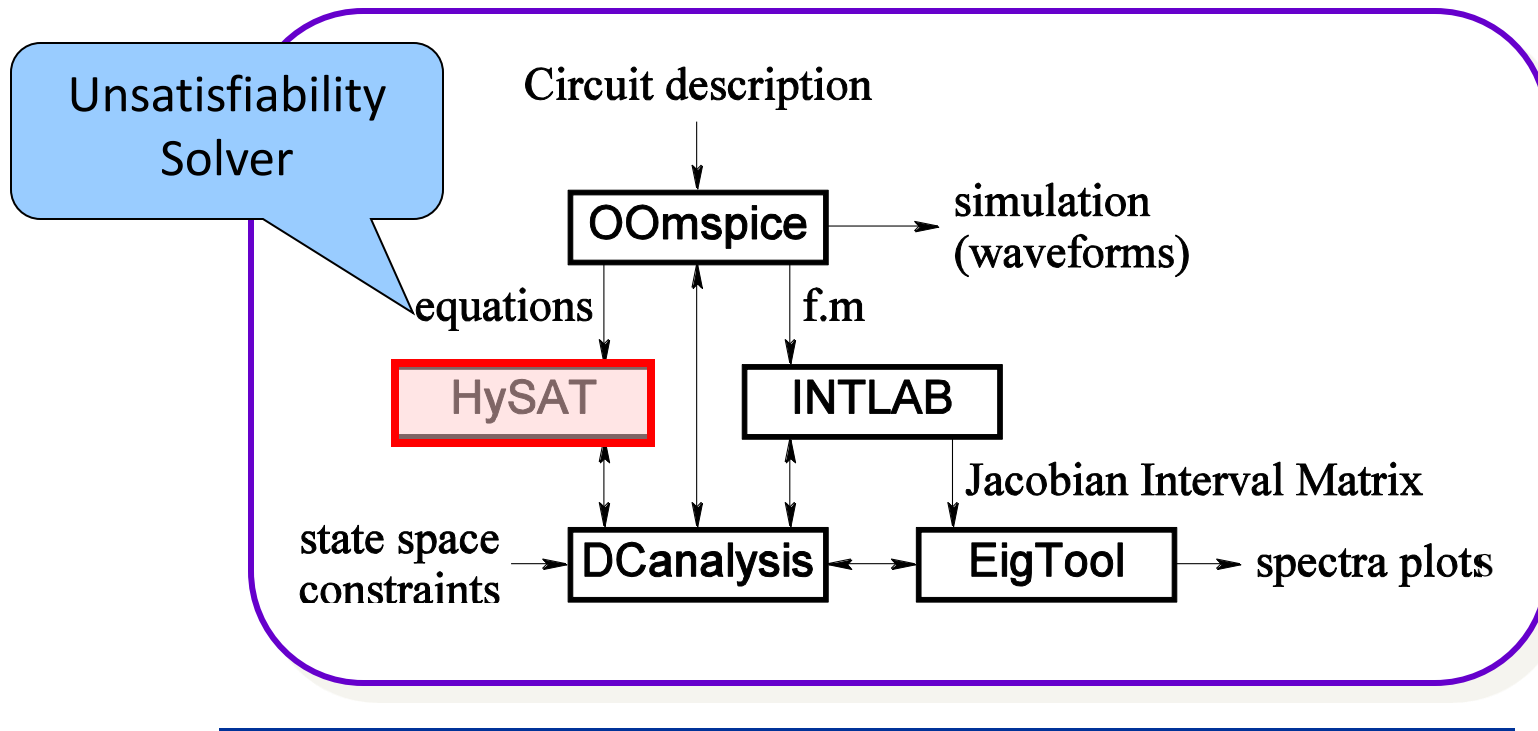


- HySAT identifies regions  $Q$  that might contain DC equilibria
- Iterative calls until HySAT establishes that the remaining space does not contain any equilibria
- Candidate regions  $Q$  forwarded to INTLAB for further analysis

# Proposed Approach

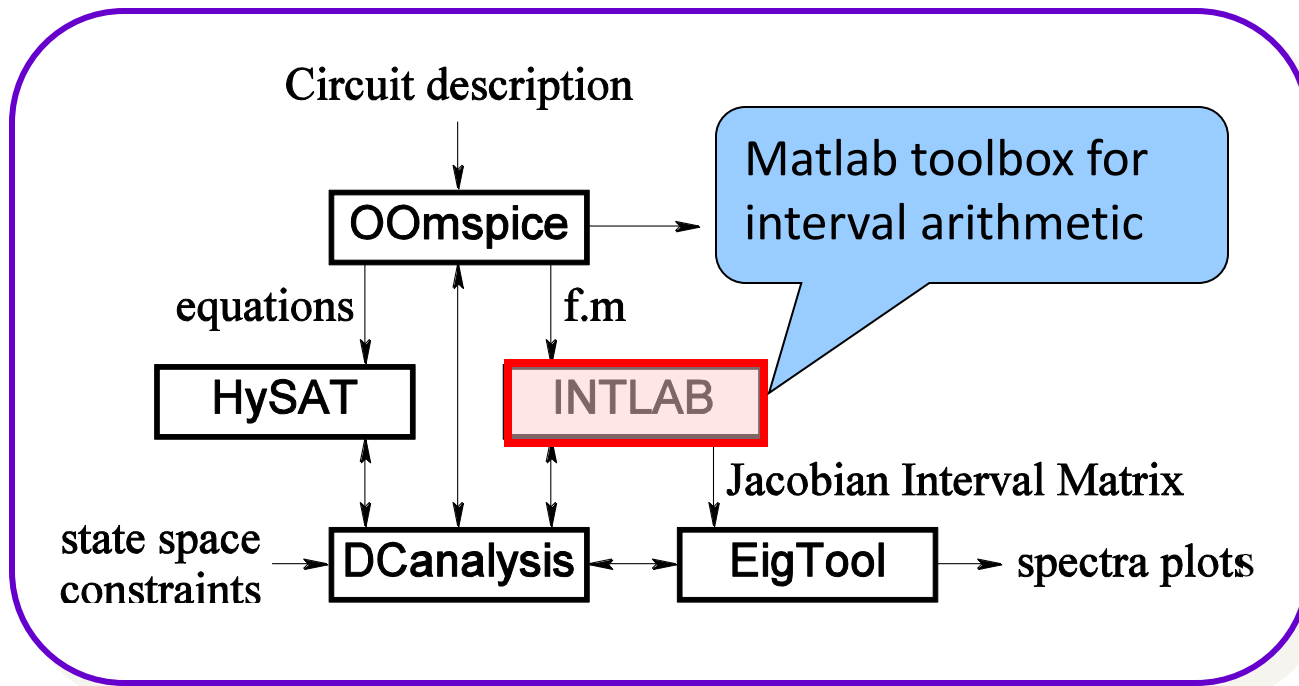


- **Refutes** regions with no DC equilibriums
- Provides **tighter** bounds for regions which includes equilibrium points
- Provides **Jacobian** Interval matrices for all points in a given region

# Proposed Approach

 

- We seek to categorize the stability of any equilibrium as definitely **stable**, definitely **unstable**, and **unknown**.
- Region does not contain a DC operating point if all matrices in provided Interval Matrix have at least one eigenvalue with **positive real** component
- Region contains a DC operating point if all matrices in provided Interval Matrix have all eigenvalues with **negative real** component

# Verification Outcome

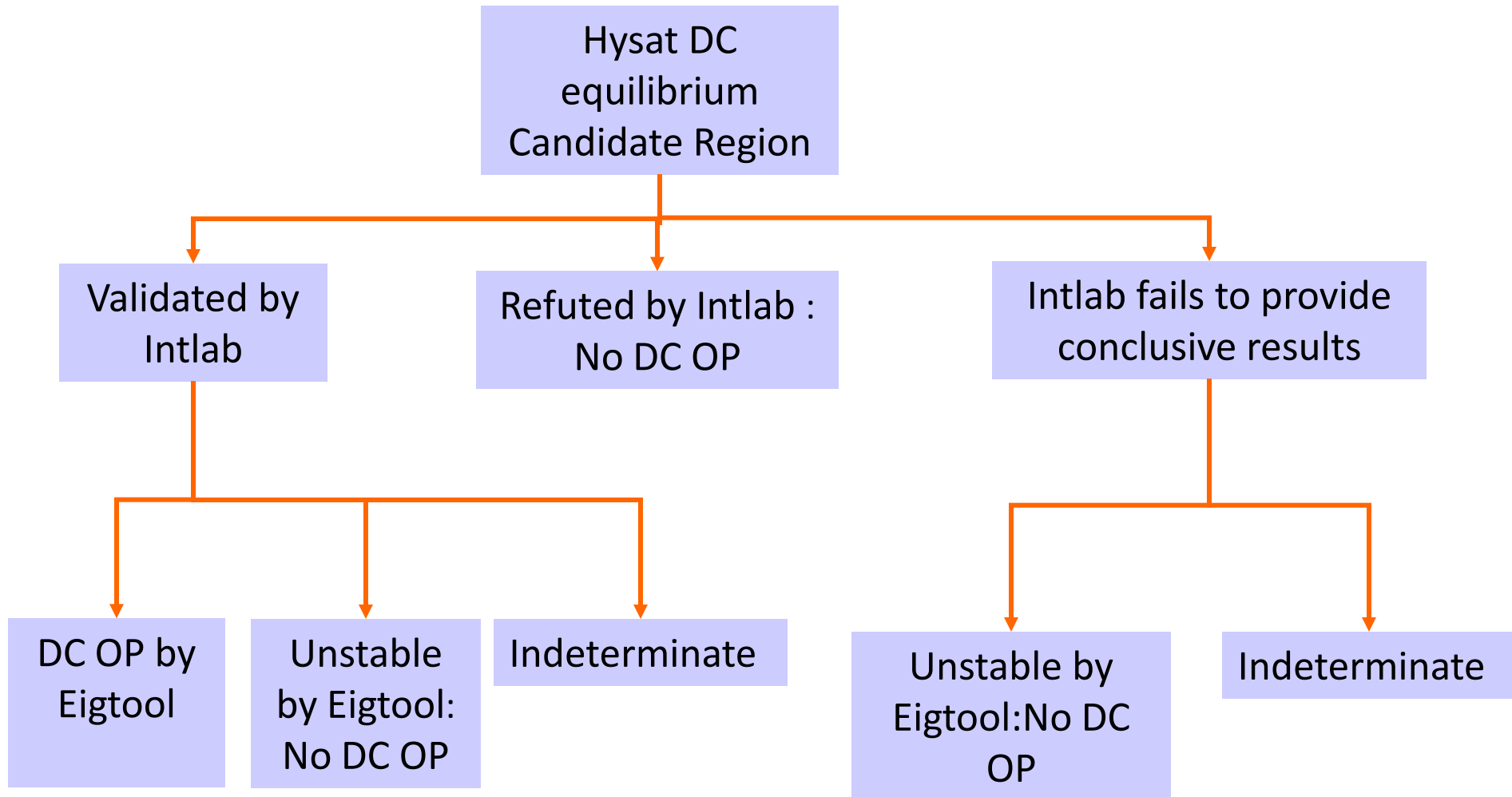

# Talk Outline

- ❑ Introduction
- ❑ Formal Verification of Circuits: An Overview
- ❑ DC Analysis:
  - ❑ Basic Concepts
  - ❑ A Formal Approach
- ❑ Case Studies
- ❑ Enhancing the Verification with invariants
- ❑ Discussion


# Schmitt Trigger

```
1 function m = Schmitt_Trigger
2
3 %Parameters for First Order Transistors model
4 trn_params = 'Trans_params';
5 % Gate, Source and Drain Capacitance
6 C = [0.55e-15, 0.55e-15/2, 0.55e-15/2];
7 % Input Signal parameters
8 Pulse_params = 'pulse_param';
9
10 Vin1 = Voltage_Source_Pulse('Vin1', Pulse_params);
11 Vdd = Supply_Voltage('Vdd', 1.8);
12 Gnd = Ground('Gnd', 0);
13 NMos1 = NmosCell('NMos1', trn_params, C);
14 PMos1 = PmosCell('PMos1', trn_params, C);
15 PC = Trans_series('PC', trn_params, C, -1);
16 NC = Trans_series('NC', trn_params, C, 1);
17
18 m = connect_pins(m, Vdd, NMos1.D, 'node_vdd');
19 m = connect_pins(m, Vdd, PC.Vs);
20 m = connect_pins(m, Gnd, PMos1.D, 'node_gnd');
21 m = connect_pins(m, PC.Vgnd, Gnd);
22 m = connect_pins(m, NC.Vgnd, Gnd);
23 m = connect_pins(m, Gnd, Vin1.N);
24 m = connect_pins(m, Gnd, NC.Vs);
25 m = connect_pins(m, PC.Out, PMos1.S, 'node_y1');
26 m = connect_pins(m, NC.Out, NMos1.S, 'node_y2');
27 m = connect_pins(m, Vin1.P, PC.In, 'node_in');
28 m = connect_pins(m, Vin1.P, NC.In);
29 m = connect_pins(m, PMos1.G, PC.Vd, 'node_out');
30 m = connect_pins(m, NMos1.G, PC.Vd);
31 m = connect_pins(m, PC.Vd, NC.Vd);
32
33 m = end_circuit(m);
```

Parameters

Components  
Instantiations

Pins  
Connections

 



# Schmitt Trigger Circuit Equations

```
1 function dydt = Schmitt_Trigger_model(t,y)
```

```
2  
3 Cap_node_out_V_Port = y(1,:);
```

```
4 Cap_node_y2_V_Port = y(2,:);
```

```
5 Cap_node_y1_V_Port = y(3,:);
```



State Space

```
6  
7 Vin1_V_Port = fun_pulse(t,'pulse_params');
```

```
8 node_gnd_V = 0;
```

```
9 node_vdd_V = 1.80;
```

```
10 node_in_V = node_gnd_V+Vin1_V_Port;
```

```
11 node_y2_V = node_gnd_V+Cap_node_y2_V_Port;
```

```
12 node_y1_V = node_gnd_V+Cap_node_y1_V_Port;
```

```
13 node_out_V = node_gnd_V+Cap_node_out_V_Port;
```

```
14 Pmos1_PC_Ids = fun_mos(node_in_V,node_vdd_V,node_y1_V,-1,'Trans_Params');
```

```
15 Nmos1_NC_Ids = fun_mos(node_in_V,node_gnd_V,node_y2_V,1,'Trans_Params');
```

```
16 Nmos2_NC_Ids = fun_mos(node_in_V,node_y2_V,node_out_V,1,'Trans_Params');
```

```
17 Pmos2_PC_Ids = fun_mos(node_in_V,node_y1_V,node_out_V,-1,'Trans_Params');
```

```
18 PMos1_Ids = fun_mos(node_out_V,node_y1_V,node_gnd_V,-1,'Trans_Params');
```

```
19 NMos1_Ids = fun_mos(node_out_V,node_y2_V,node_vdd_V,1,'Trans_Params');
```

```
20 Cap_node_out_I_Port = -Pmos2_PC_Ids-Nmos2_NC_Ids;
```

```
21 Cap_node_y2_I_Port = -Nmos1_NC_Ids+Nmos2_NC_Ids+NMos1_Ids;
```

```
22 Cap_node_y1_I_Port = -Pmos1_PC_Ids+Pmos2_PC_Ids+PMos1_Ids;
```

```
23  
24 dydt = [Cap_node_out_I_Port/1.650000e-15;...
```

```
25         Cap_node_y2_I_Port/8.250000e-16;...
```

```
26         Cap_node_y1_I_Port/8.250000e-16];
```

Equations




KCL





ODEs

# Schmitt Trigger

 

Schematic

  

DC transfer Function


Hysteresis

Narrow inconclusive bounds width of **0.007** and **0.006** in  $[0, 1.8]$

# Schmitt Trigger

## DC Operating Points


Vin = 1.8 V

 

dim = 3


Bounds on eigenvalue

Eigenvalue of central matrix

 


Norm of Offset Matrix (log scale)

 Jacobian Interval Matrix = Central Matrix +/- Offset Matrix




# Schmitt Trigger

## DC Operating Points

 


$V_{in} = 0$  V

## Unstable Equilibria: Not DC OP

 


$V_{in} = 1$  V

## Indeterminate case

 


$V_{in} = 1.124$  V

 


 
## Other Experimental Results:

- Proved that **Ring** Oscillators with **odd number** of stages (up to 25 stages) do not possess DC operating points
- Effect of **load capacitance** on the oscillation. Sufficient large capacitance load **can break** the oscillation




- Proved that **Even** number of Ring oscillators (up to 24 stages) always have stable state

# Ring Oscillator: 3 and 25 stages

  


# Rambus Oscillators

 


*For a given choice of transistor sizes, show that the circuit operates properly for “almost all” initial conditions*

# Rambus Oscillators


DC Operating Points

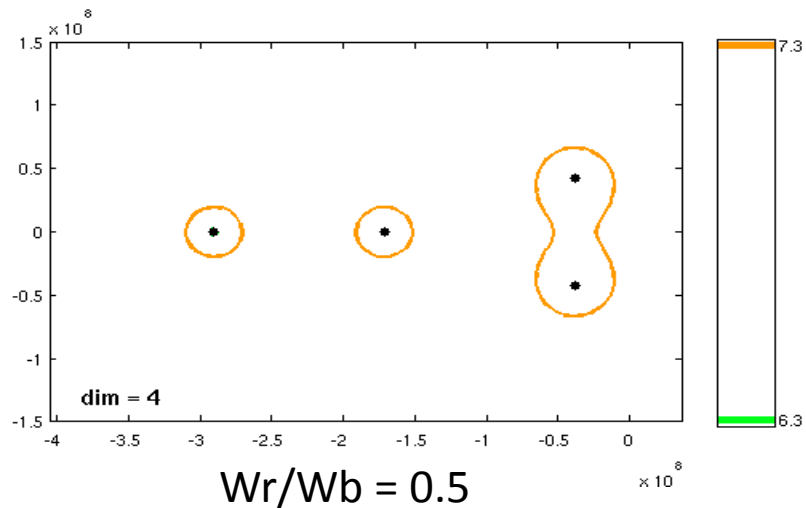


Indeterminate

 

Unstable Equilibria : Not DC OP

 

DC Operating Points

 



# Talk Outline

- ❑ Introduction
- ❑ Formal Verification of Circuits: An Overview
- ❑ DC Analysis:
  - ❑ Basic Concepts
  - ❑ A Formal Approach
- ❑ Case Studies
- ❑ Enhancing the Verification with invariants
- ❑ Discussion

# Invariant Checking

- Find upper and lower bounds on the operating state space.
- Given a constraint, is it a bound on the state space?
- For each state variable  $x$ :



find  $b1$  and  $b2$  such that:

$$x = b2 \text{ implies } \dot{x} \leq 0$$



and

$$x = b1 \text{ implies } \dot{x} \geq 0$$

# Invariant Checking: Schmitt Trigger

  


# Invariant Checking: Schmitt Trigger

  

**y2 Bounds**

# Invariant Checking: Schmitt Trigger

## Problems with First Order Model

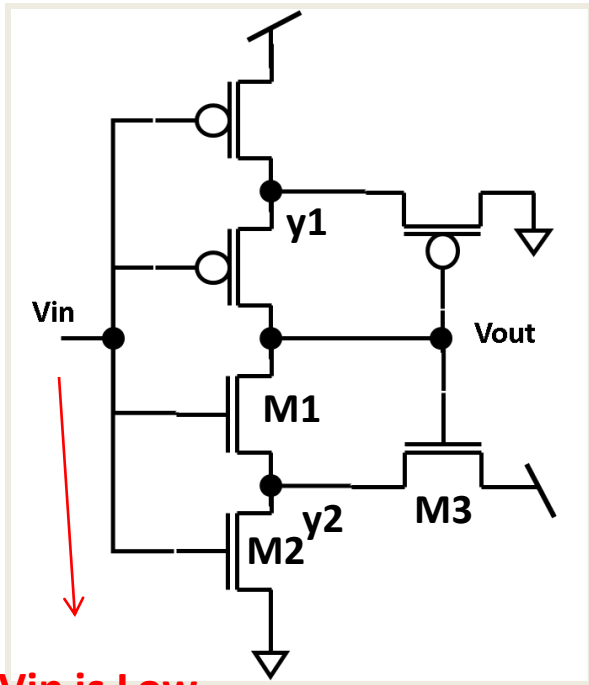


Vin is Low

➔ M1 and M2 are off

Suppose Initial  $V_{y2} > b2$

➔ M3:  $V_{gs} < v_{th}$  and M3 is off

 

• First order model does not consider subthreshold current (no leakage)


• Failure to prove bounds on voltage nodes for some input voltages

# EKV Mosfet Model

- MOS model that provides a similar behavioral representation compared to spice models
- **EKV Model** is accurate even when the MOSFET is operating in the subthreshold region
- Closed form expressions that are continuous across the transistor operating regions.
- **Hysat** friendly

# Invariant Checking: Schmitt Trigger

## EKV Model

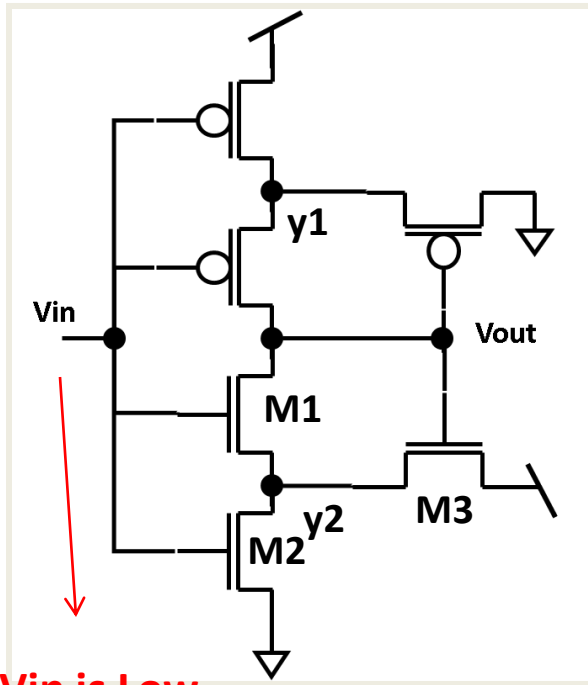


Vin is Low

➔ M1 and M2 are off

Suppose Initial  $V_{y2} > b2$

➔ M2:  $V_{gs} < v_{th}$  and M2 is off

 

•EKV mode considers subthreshold current (no leakage)

•Bounds were proved automatically

# Talk Outline

- ❑ Introduction
- ❑ Formal Verification of Circuits: An Overview
- ❑ DC Analysis:
  - ❑ Basic Concepts
  - ❑ A Formal Approach
- ❑ Case Studies
- ❑ Enhancing the Verification with invariants
- ❑ Discussion



# Challenges Outlined in FMACD'08 Talk on Open Analog Problems

- Avoiding transient simulation
- Establishing that operating point assumptions are valid
- Establishing that all initial conditions result in correct behavior
- Dealing with non-linearity

# Conclusion

- Tackling DC analysis in a more formalized way
- Identifying and classifying DC operating points of circuits using a collection of tools in the open domain
- Demonstrating the presented methodology on a variety of circuits

**Is formal verification possible for Analog Designs?**

**Formal methods is possible. But is it effective??**

***Primary Results say YES***

I've got this pain in all  
the diodes down my  
left side\*.



*\* From the Hitchhiker's Guide to the Galaxy, by Douglas Adams*