

UBC Physics 102

Lecture 8

Rik Blok



Outline

- ▷ Capacitors
- ▷ Capacitance
- ▷ Series and parallel
- ▷ Energy storage
- ▷ Dielectrics
- ▷ Electric current
- ▷ Ohm's law
- ▷ Resistivity
- ▷ End

Capacitors [Text: Sect. 24-1]

● **Definition:** *Capacitor*

Capacitors [Text: Sect. 24-1]


● **Definition:** *Capacitor*

- Device that can store electric charge.

Capacitors [Text: Sect. 24-1]

● **Definition:** *Capacitor*

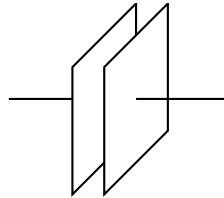
- Device that can store electric charge.
- Often constructed of two parallel plates.



Capacitors [Text: Sect. 24-1]

● **Definition:** *Capacitor*

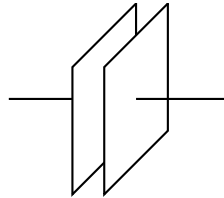- Device that can store electric charge.
- Often constructed of two parallel plates.





- Circuit diagram symbol: 

Capacitors [Text: Sect. 24-1]

● Definition: *Capacitor*

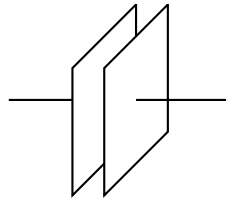- Device that can store electric charge.
- Often constructed of two parallel plates.



- Circuit diagram symbol: 
- When voltage V applied to plates they acquire charges $\pm Q$ where

$$Q = CV.$$

Capacitance [Text: Sect. 24-2]

● **Definition:** *Capacitance*, C

Capacitance [Text: Sect. 24-2]

- **Definition:** *Capacitance*, C
 - Constant of proportionality.

Capacitance [Text: Sect. 24-2]

- **Definition:** *Capacitance*, C
 - Constant of proportionality.
 - Depends on details of capacitor (eg. size, shape).

Capacitance [Text: Sect. 24-2]

- **Definition:** *Capacitance*, C
 - Constant of proportionality.
 - Depends on details of capacitor (eg. size, shape).
- **Unit: Farad, F**

Capacitance [Text: Sect. 24-2]

- **Definition:** *Capacitance*, C
 - Constant of proportionality.
 - Depends on details of capacitor (eg. size, shape).
- **Unit: Farad**, F
 - Unit of capacitance,

$$1 F = 1 C/V.$$

Capacitance [Text: Sect. 24-2]

- **Definition:** *Capacitance*, C

- Constant of proportionality.
- Depends on details of capacitor (eg. size, shape).

- **Unit: Farad, F**

- Unit of capacitance,

$$1 \text{ F} = 1 \text{ C/V}.$$

- **Discussion: Capacitance**

Capacitance [Text: Sect. 24-2]

● Definition: *Capacitance*, C

- Constant of proportionality.
- Depends on details of capacitor (eg. size, shape).

● Unit: Farad, F

- Unit of capacitance,


$$1 \text{ F} = 1 \text{ C/V}.$$

● Discussion: Capacitance

- To derive capacitance solve for relationship between V and Q . Will find $Q \propto V$. C is proportionality constant.


Capacitance, contd

• Derivation: Parallel plate capacitance

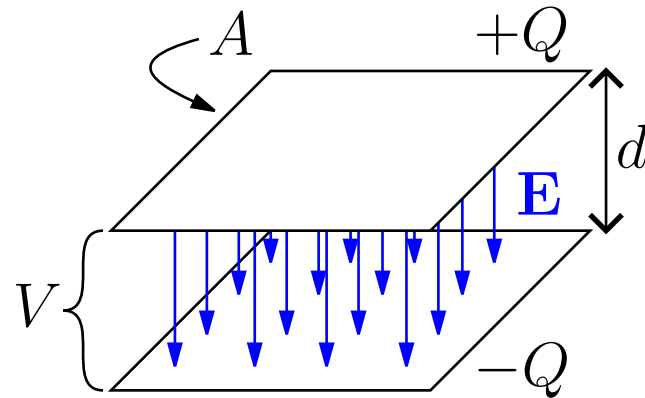

Capacitance, contd

• Derivation: Parallel plate capacitance

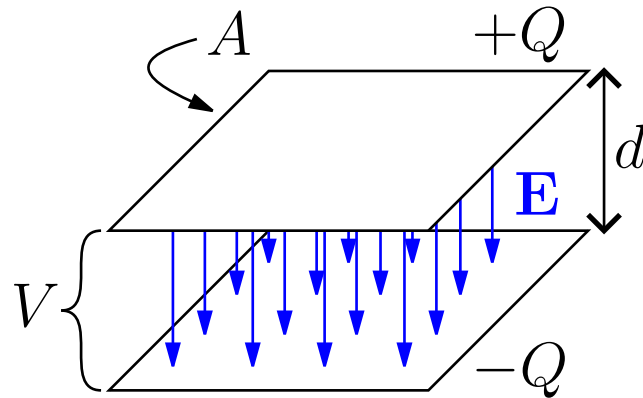


- From Gauss's law can find strength of E -field between plates,

$$E = \frac{\sigma}{\epsilon_0}.$$

Capacitance, contd

• Derivation: Parallel plate capacitance

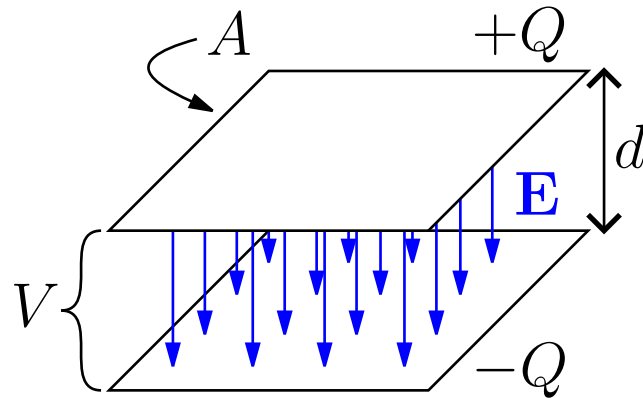

- From Gauss's law can find strength of E -field between plates,

$$E = \frac{\sigma}{\epsilon_0}.$$

- σ is surface charge density, $\sigma = \frac{Q}{A}$.

Capacitance, contd

• Derivation: Parallel plate capacitance, contd

Capacitance, contd

• Derivation: Parallel plate capacitance, contd

- E uniform so can use $V = -E_l l$ (ignoring sign) to get

$$V = \frac{\sigma d}{\epsilon_0} = \frac{Qd}{\epsilon_0 A}.$$

Capacitance, contd

• Derivation: Parallel plate capacitance, contd

- E uniform so can use $V = -E_l l$ (ignoring sign) to get

$$V = \frac{\sigma d}{\epsilon_0} = \frac{Qd}{\epsilon_0 A}.$$

- Rearranging gives $Q = \frac{\epsilon_0 A}{d} V = CV$ so

$$C = \frac{\epsilon_0 A}{d}.$$

Capacitance, contd

• Derivation: Parallel plate capacitance, contd

- E uniform so can use $V = -E_l l$ (ignoring sign) to get

$$V = \frac{\sigma d}{\epsilon_0} = \frac{Qd}{\epsilon_0 A}.$$

- Rearranging gives $Q = \frac{\epsilon_0 A}{d} V = CV$ so

$$C = \frac{\epsilon_0 A}{d}.$$

- Can use similar method for other shapes.

Series and parallel [Text: Sect. 24-3]

● Discussion: Review of circuit diagrams

Series and parallel [Text: Sect. 24-3]

- **Discussion: Review of circuit diagrams**
 - Lines are wires connecting components. No voltage drop.

Series and parallel [Text: Sect. 24-3]

- **Discussion: Review of circuit diagrams**
 - Lines are wires connecting components. No voltage drop.
 - Battery (Symbol: $\begin{array}{c} + \\ | \\ - \end{array}$) raises voltage on + side. (Analogy: an escalator.)

Series and parallel [Text: Sect. 24-3]

● Discussion: Review of circuit diagrams

- Lines are wires connecting components. No voltage drop.
- Battery (Symbol: $\begin{smallmatrix} + & \text{---} & | & \text{---} & - \end{smallmatrix}$) raises voltage on $+$ side. (Analogy: an escalator.)
- Capacitor: $\begin{smallmatrix} | & \text{---} & | \end{smallmatrix}$

Series and parallel [Text: Sect. 24-3]


● Discussion: Review of circuit diagrams

- Lines are wires connecting components. No voltage drop.
- Battery (Symbol: $\begin{smallmatrix} + & - \\ | & | \end{smallmatrix}$) raises voltage on $+$ side. (Analogy: an escalator.)
- Capacitor: $\begin{smallmatrix} | & | \\ \text{---} & \text{---} \end{smallmatrix}$
- Voltage pumps charge onto plates.

Series and parallel [Text: Sect. 24-3]

● Discussion: Review of circuit diagrams

- Lines are wires connecting components. No voltage drop.
- Battery (Symbol: $\begin{array}{c} + \\ | \\ - \end{array}$) raises voltage on $+$ side.
(Analogy: an escalator.)
- Capacitor: $\begin{array}{c} | \\ | \end{array}$
- Voltage pumps charge onto plates.
- Net voltage change over any loop must be zero.
(Analogy: net height change = 0.)

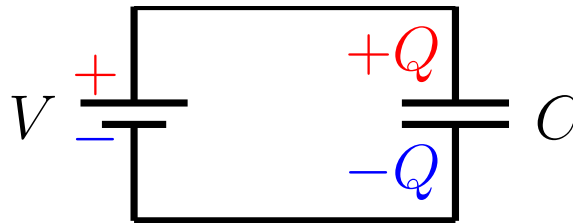

Series and parallel, contd

● Definition: *Parallel*

Series and parallel, contd

● **Definition:** *Parallel*

- Path splits, goes across multiple components, and rejoins.

Series and parallel, contd

● **Definition:** *Parallel*


- Path splits, goes across multiple components, and rejoins.
- Voltage drop identical across each path.

Series and parallel, contd

● Definition: *Parallel*

- Path splits, goes across multiple components, and rejoins.
- Voltage drop identical across each path.

● Derivation: Parallel capacitors

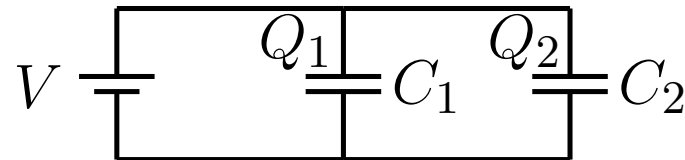


Series and parallel, contd

● Definition: *Parallel*

- Path splits, goes across multiple components, and rejoins.
- Voltage drop identical across each path.

● Derivation: Parallel capacitors

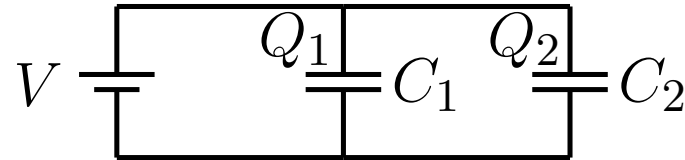


- Same voltage drop across each capacitor so $V_1 = V_2 = V$.

Series and parallel, contd

● Definition: *Parallel*

- Path splits, goes across multiple components, and rejoins.
- Voltage drop identical across each path.

● Derivation: Parallel capacitors

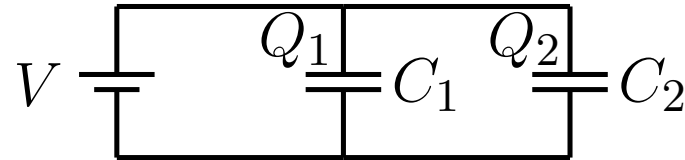

- Same voltage drop across each capacitor so $V_1 = V_2 = V$.
- Charge on capacitors: $Q_1 = C_1V$, $Q_2 = C_2V$.

Series and parallel, contd

• Derivation: Parallel capacitors, contd

Series and parallel, contd

• Derivation: Parallel capacitors, contd

- Total charge Q pumped onto both capacitors,

$$\begin{aligned} Q &= Q_1 + Q_2 = C_1 V + C_2 V \\ &= (C_1 + C_2) V. \end{aligned}$$

Series and parallel, contd

• Derivation: Parallel capacitors, contd

- Total charge Q pumped onto both capacitors,

$$\begin{aligned} Q &= Q_1 + Q_2 = C_1V + C_2V \\ &= (C_1 + C_2)V. \end{aligned}$$

- Equivalent to a single capacitor, $Q = C_{eq}V$, where

$$C_{eq} = C_1 + C_2.$$

Series and parallel, contd

• Derivation: Parallel capacitors, contd

- Total charge Q pumped onto both capacitors,

$$\begin{aligned} Q &= Q_1 + Q_2 = C_1 V + C_2 V \\ &= (C_1 + C_2) V. \end{aligned}$$

- Equivalent to a single capacitor, $Q = C_{eq} V$, where

$$C_{eq} = C_1 + C_2.$$

• Definition: *Series*

Series and parallel, contd

● Derivation: Parallel capacitors, contd

- Total charge Q pumped onto both capacitors,

$$\begin{aligned} Q &= Q_1 + Q_2 = C_1V + C_2V \\ &= (C_1 + C_2)V. \end{aligned}$$

- Equivalent to a single capacitor, $Q = C_{eq}V$, where

$$C_{eq} = C_1 + C_2.$$

● Definition: *Series*

- Components are connected end to end.

Series and parallel, contd

● Derivation: Parallel capacitors, contd

- Total charge Q pumped onto both capacitors,

$$\begin{aligned} Q &= Q_1 + Q_2 = C_1V + C_2V \\ &= (C_1 + C_2)V. \end{aligned}$$

- Equivalent to a single capacitor, $Q = C_{eq}V$, where


$$C_{eq} = C_1 + C_2.$$

● Definition: *Series*

- Components are connected end to end.
- Total voltage drop is sum of all components.


Series and parallel, contd

• Derivation: Series capacitors

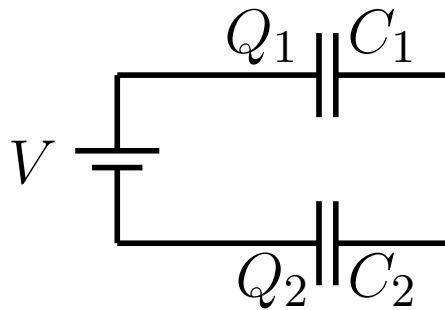

Series and parallel, contd


• Derivation: Series capacitors

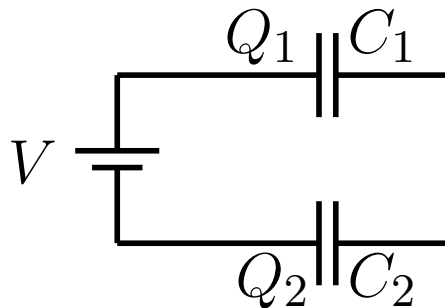

- Charge conserved so + charge built up on capacitor 1 must leave – charge on capacitor 2, and vice versa.

Series and parallel, contd


• Derivation: Series capacitors

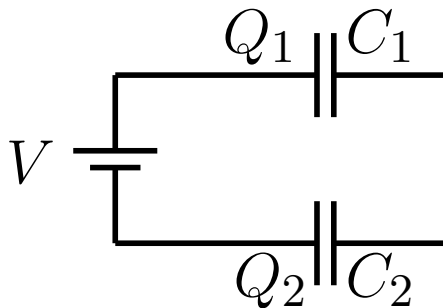

- Charge conserved so + charge built up on capacitor 1 must leave – charge on capacitor 2, and vice versa.
- So charge the same on both capacitors,
 $Q_1 = Q_2 = Q$.

Series and parallel, contd

● Derivation: Series capacitors

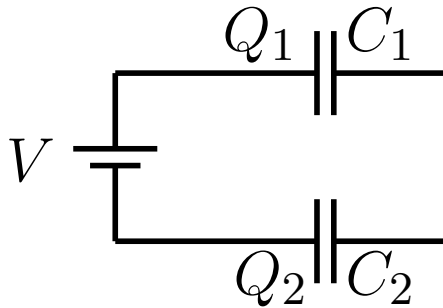

- Charge conserved so + charge built up on capacitor 1 must leave – charge on capacitor 2, and vice versa.
- So charge the same on both capacitors,
 $Q_1 = Q_2 = Q$.
- Voltage drop across capacitors: $V_1 = \frac{Q}{C_1}$, $V_2 = \frac{Q}{C_2}$.

Series and parallel, contd

• Derivation: Series capacitors, contd

Series and parallel, contd

• Derivation: Series capacitors, contd

- Total voltage drop across capacitors equal to voltage climb across battery,

$$\begin{aligned} V &= V_1 + V_2 = \frac{Q}{C_1} + \frac{Q}{C_2} \\ &= \left(\frac{1}{C_1} + \frac{1}{C_2} \right) Q. \end{aligned}$$

Series and parallel, contd

● Derivation: Series capacitors, contd

- Total voltage drop across capacitors equal to voltage climb across battery,

$$\begin{aligned} V &= V_1 + V_2 = \frac{Q}{C_1} + \frac{Q}{C_2} \\ &= \left(\frac{1}{C_1} + \frac{1}{C_2} \right) Q. \end{aligned}$$

- Equivalent to a single capacitor, $V = \frac{1}{C_{eq}} Q$, where

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}.$$

Series and parallel, contd

● Discussion: Series and parallel capacitors

Series and parallel, contd

- **Discussion: Series and parallel capacitors**
 - Can use these “replacement” rules to simplify complex configurations of capacitors.

Series and parallel, contd

● Discussion: Series and parallel capacitors

- Can use these “replacement” rules to simplify complex configurations of capacitors.
- Rarely not able to divide circuit into series and parallel. But voltage rules (eg. $\oint \vec{E} \cdot d\vec{l} = 0$ over loop), charge conservation, and other laws still apply.

Series and parallel, contd

- **Discussion: Series and parallel capacitors**
 - Can use these “replacement” rules to simplify complex configurations of capacitors.
 - Rarely not able to divide circuit into series and parallel. But voltage rules (eg. $= 0$ over loop), charge conservation, and other laws still apply.
- **Interactive Quiz: PRS 08a**

Energy storage [Text: Sect. 24-4]

● Discussion: Energy storage

Energy storage [Text: Sect. 24-4]

- **Discussion: Energy storage**
 - Have to do work to charge capacitor.

Energy storage [Text: Sect. 24-4]

- **Discussion: Energy storage**
 - Have to do work to charge capacitor.
 - Work stored as potential energy in capacitor.

Energy storage [Text: Sect. 24-4]

● Discussion: Energy storage

- Have to do work to charge capacitor.
- Work stored as potential energy in capacitor.
- Energy stored in electric field (between plates).

Energy storage [Text: Sect. 24-4]

● Discussion: Energy storage

- Have to do work to charge capacitor.
- Work stored as potential energy in capacitor.
- Energy stored in electric field (between plates).

● Derivation: Potential energy

Energy storage [Text: Sect. 24-4]

● Discussion: Energy storage

- Have to do work to charge capacitor.
- Work stored as potential energy in capacitor.
- Energy stored in electric field (between plates).

● Derivation: Potential energy

- Can derive how much energy stored in capacitor.

Energy storage [Text: Sect. 24-4]

● Discussion: Energy storage

- Have to do work to charge capacitor.
- Work stored as potential energy in capacitor.
- Energy stored in electric field (between plates).

● Derivation: Potential energy

- Can derive how much energy stored in capacitor.
- Consider situation where voltage \hat{V} ramped up gradually from $\hat{V} = 0$ to $\hat{V} = V$.

Energy storage [Text: Sect. 24-4]

● Discussion: Energy storage

- Have to do work to charge capacitor.
- Work stored as potential energy in capacitor.
- Energy stored in electric field (between plates).

● Derivation: Potential energy

- Can derive how much energy stored in capacitor.
- Consider situation where voltage \hat{V} ramped up gradually from $\hat{V} = 0$ to $\hat{V} = V$.
- Charge on plates when ramp voltage is \hat{V} is $Q = C\hat{V}$.

Energy storage [Text: Sect. 24-4]

● Discussion: Energy storage

- Have to do work to charge capacitor.
- Work stored as potential energy in capacitor.
- Energy stored in electric field (between plates).

● Derivation: Potential energy

- Can derive how much energy stored in capacitor.
- Consider situation where voltage \hat{V} ramped up gradually from $\hat{V} = 0$ to $\hat{V} = V$.
- Charge on plates when ramp voltage is \hat{V} is $Q = C\hat{V}$.
- Recall, energy of charge Q at voltage \hat{V} is $U = Q\hat{V}$.

Energy storage [Text: Sect. 24-4]

● Discussion: Energy storage

- Have to do work to charge capacitor.
- Work stored as potential energy in capacitor.
- Energy stored in electric field (between plates).

● Derivation: Potential energy

- Can derive how much energy stored in capacitor.
- Consider situation where voltage \hat{V} ramped up gradually from $\hat{V} = 0$ to $\hat{V} = V$.
- Charge on plates when ramp voltage is \hat{V} is $Q = C\hat{V}$.
- Recall, energy of charge Q at voltage \hat{V} is $U = Q\hat{V}$.
- But both Q and \hat{V} changing so can't use $U = QV$.

Energy storage, contd

• Derivation: Potential energy, contd

Energy storage, contd

• Derivation: Potential energy, contd

- But if voltage change small enough ($d\hat{V} \rightarrow 0$) then can assume Q constant over change.

Energy storage, contd

• Derivation: Potential energy, contd

- But if voltage change small enough ($d\hat{V} \rightarrow 0$) then can assume Q constant over change.
- Increase in potential energy is

$$dU = Q d\hat{V} = C\hat{V} d\hat{V}.$$

Energy storage, contd

• Derivation: Potential energy, contd

- But if voltage change small enough ($d\hat{V} \rightarrow 0$) then can assume Q constant over change.
- Increase in potential energy is

$$dU = Q d\hat{V} = C\hat{V} d\hat{V}.$$

- Total potential is sum of increments, $U = \int_0^V C\hat{V} d\hat{V},$

$$U = \frac{1}{2}CV^2 = \frac{1}{2}\frac{Q^2}{C}.$$

Dielectrics [Text: Sect. 24-5]

- **Definition:** *Dielectric constant, K*

Dielectrics [Text: Sect. 24-5]

- **Definition:** *Dielectric constant, K*
 - Amount by which material between plates increases capacitance,

$$C = KC_0.$$

Dielectrics [Text: Sect. 24-5]

- **Definition:** *Dielectric constant, K*

- Amount by which material between plates increases capacitance,

$$C = KC_0.$$

- C_0 is capacitance in vacuum (or air, roughly).

Dielectrics [Text: Sect. 24-5]

● **Definition:** *Dielectric constant, K*

- Amount by which material between plates increases capacitance,

$$C = KC_0.$$

- C_0 is capacitance in vacuum (or air, roughly).
- $K > 1$ for dielectric.

Dielectrics [Text: Sect. 24-5]

● **Definition:** *Dielectric constant, K*

- Amount by which material between plates increases capacitance,

$$C = KC_0.$$

- C_0 is capacitance in vacuum (or air, roughly).
- $K > 1$ for dielectric.
- Dielectric works by polarizing, setting up electric field contrary to original.

Dielectrics [Text: Sect. 24-5]

● **Definition:** *Dielectric constant, K*

- Amount by which material between plates increases capacitance,

$$C = KC_0.$$

- C_0 is capacitance in vacuum (or air, roughly).
- $K > 1$ for dielectric.
- Dielectric works by polarizing, setting up electric field contrary to original.
- Changing C changes potential energy U capacitor will hold.

Dielectrics, contd

● Interactive Quiz: PRS 08b

Dielectrics, contd

- **Interactive Quiz: PRS 08b**
- **Example: Pr. 75**

Dielectrics, contd

- **Interactive Quiz: PRS 08b**
- **Example: Pr. 75**
 - A parallel-plate capacitor is isolated with a charge $\pm Q$ on each plate. If the separation of the plates is halved and a dielectric (constant K) is inserted in place of air, by what factor does the energy storage change? To what do you attribute the change in stored potential energy?

Dielectrics, contd

- **Interactive Quiz: PRS 08b**
- **Example: Pr. 75**
 - A parallel-plate capacitor is isolated with a charge $\pm Q$ on each plate. If the separation of the plates is halved and a dielectric (constant K) is inserted in place of air, by what factor does the energy storage change? To what do you attribute the change in stored potential energy?
- **Solution: Pr. 75**

Dielectrics, contd

- **Interactive Quiz: PRS 08b**

- **Example: Pr. 75**

- A parallel-plate capacitor is isolated with a charge $\pm Q$ on each plate. If the separation of the plates is halved and a dielectric (constant K) is inserted in place of air, by what factor does the energy storage change? To what do you attribute the change in stored potential energy?

- **Solution: Pr. 75**

- We know charge Q held constant.

Dielectrics, contd

● Solution: Pr. 75, contd

Dielectrics, contd

● Solution: Pr. 75, contd

● So $\boxed{U = \frac{1}{2} \frac{Q^2}{C}}$ gives potential energy. Initially,

$$U_0 = \frac{1}{2} \frac{Q^2}{C_0}.$$

Dielectrics, contd

● Solution: Pr. 75, contd

- So $\boxed{U = \frac{1}{2} \frac{Q^2}{C}}$ gives potential energy. Initially,

$$U_0 = \frac{1}{2} \frac{Q^2}{C_0}.$$

- Let's think about this in 2 steps:

Dielectrics, contd

● Solution: Pr. 75, contd

- So $\boxed{U = \frac{1}{2} \frac{Q^2}{C}}$ gives potential energy. Initially,

$$U_0 = \frac{1}{2} \frac{Q^2}{C_0}.$$

- Let's think about this in 2 steps:
- Step 1: halving the separation.

Dielectrics, contd

● Solution: Pr. 75, contd

- So $\boxed{U = \frac{1}{2} \frac{Q^2}{C}}$ gives potential energy. Initially,

$$U_0 = \frac{1}{2} \frac{Q^2}{C_0}.$$

- Let's think about this in 2 steps:
- Step 1: halving the separation.
- From $\boxed{C = \frac{\epsilon_0 A}{d}}$ this has the effect of doubling the capacitance,

$$C_1 = 2C_0.$$

Dielectrics, contd

● Solution: Pr. 75, contd

Dielectrics, contd

- **Solution: Pr. 75, contd**
 - Step 2: inserting the dielectric.

Dielectrics, contd

● Solution: Pr. 75, contd

- Step 2: inserting the dielectric.
- From $C = KC_0$ the capacitance is increased by a factor K ,

$$C_2 = KC_1 = 2KC_0.$$

Dielectrics, contd

● Solution: Pr. 75, contd

- Step 2: inserting the dielectric.
- From $C = KC_0$ the capacitance is increased by a factor K ,

$$C_2 = KC_1 = 2KC_0.$$

- Now the potential energy is

$$U_2 = \frac{1}{2} \frac{Q^2}{C_2} = \frac{1}{2K} U_0.$$

Dielectrics, contd

● Solution: Pr. 75, contd

- Step 2: inserting the dielectric.
- From $C = KC_0$ the capacitance is increased by a factor K ,

$$C_2 = KC_1 = 2KC_0.$$

- Now the potential energy is

$$U_2 = \frac{1}{2} \frac{Q^2}{C_2} = \frac{1}{2K} U_0.$$

- So potential energy decreases by ratio of $2K$.

Dielectrics, contd

● Solution: Pr. 75, contd

- Step 2: inserting the dielectric.
- From $C = KC_0$ the capacitance is increased by a factor K ,

$$C_2 = KC_1 = 2KC_0.$$

- Now the potential energy is

$$U_2 = \frac{1}{2} \frac{Q^2}{C_2} = \frac{1}{2K} U_0.$$

- So potential energy decreases by ratio of $2K$.
- In each step, the potential energy decreased.

Dielectrics, contd

● Solution: Pr. 75, contd

- Step 2: inserting the dielectric.
- From $C = KC_0$ the capacitance is increased by a factor K ,

$$C_2 = KC_1 = 2KC_0.$$


- Now the potential energy is

$$U_2 = \frac{1}{2} \frac{Q^2}{C_2} = \frac{1}{2K} U_0.$$

- So potential energy decreases by ratio of $2K$.
- In each step, the potential energy decreased.
- So both changes happened spontaneously.


Dielectrics, contd

● Solution: Pr. 75, contd

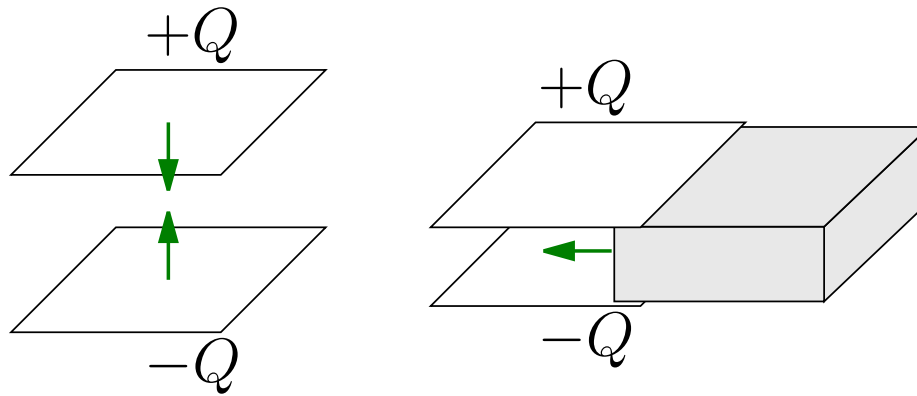

Dielectrics, contd


● Solution: Pr. 75, contd

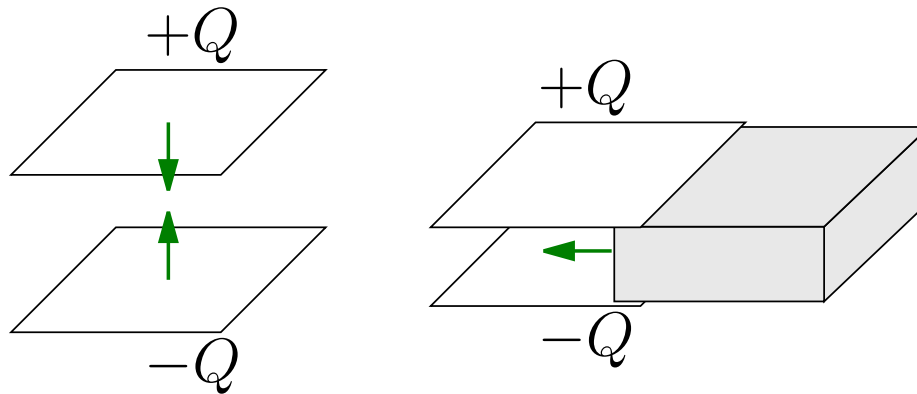

- Step 1: Releasing plates allowed them to move closer together (attraction of plates).

Dielectrics, contd

● Solution: Pr. 75, contd

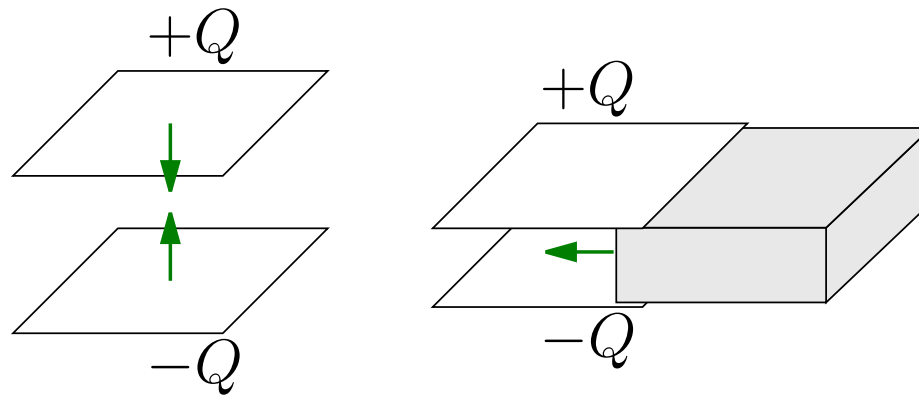

- Step 1: Releasing plates allowed them to move closer together (attraction of plates).
- Step 2: Capacitor drew in dielectric when we brought it close (dielectric polarized in proximity of capacitor then attracted to it).



Electric current [Text: Sect. 25-2]

- **Definition:** *Electric current, I*

Electric current [Text: Sect. 25-2]

- **Definition:** *Electric current, I*
 - Rate of charge flow past a point,

$$I = \frac{dQ}{dt}.$$

Electric current [Text: Sect. 25-2]

- **Definition:** *Electric current, I*
 - Rate of charge flow past a point,

$$I = \frac{dQ}{dt}.$$

- Current flows if voltage different between points.

Electric current [Text: Sect. 25-2]

- **Definition:** *Electric current, I*
 - Rate of charge flow past a point,

$$I = \frac{dQ}{dt}.$$

- Current flows if voltage different between points.
- Analogy: voltage \leftrightarrow height, current \leftrightarrow river current.

Electric current [Text: Sect. 25-2]

- **Definition:** *Electric current, I*
 - Rate of charge flow past a point,

$$I = \frac{dQ}{dt}.$$

- Current flows if voltage different between points.
 - Analogy: voltage \leftrightarrow height, current \leftrightarrow river current.
- **Unit: Ampere, A**

Electric current [Text: Sect. 25-2]

- **Definition:** *Electric current, I*

- Rate of charge flow past a point,

$$I = \frac{dQ}{dt}.$$

- Current flows if voltage different between points.
- Analogy: voltage \leftrightarrow height, current \leftrightarrow river current.

- **Unit: Ampere, A**

- Unit of current

$$1 \text{ A} = 1 \text{ C/s}.$$

Electric current, contd

● Discussion: Convention

Electric current, contd


● Discussion: Convention

- Current said to flow from high potential to low (historical).

Electric current, contd

● Discussion: Convention

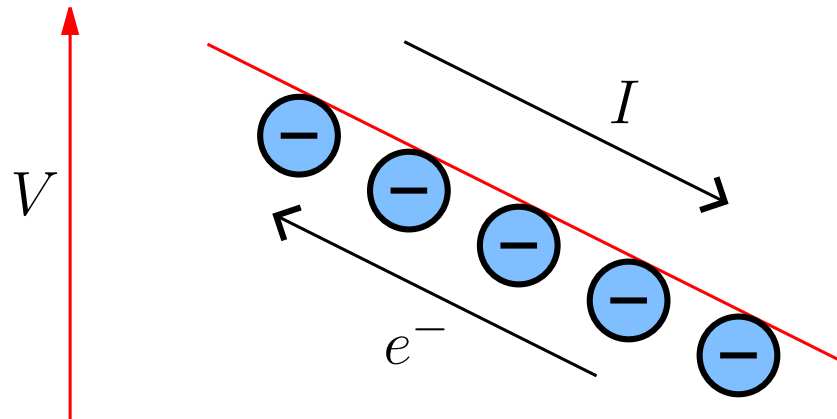
- Current said to flow from high potential to low (historical).
- Actually, electrons flowing from low to high.



Electric current, contd

Discussion: Convention

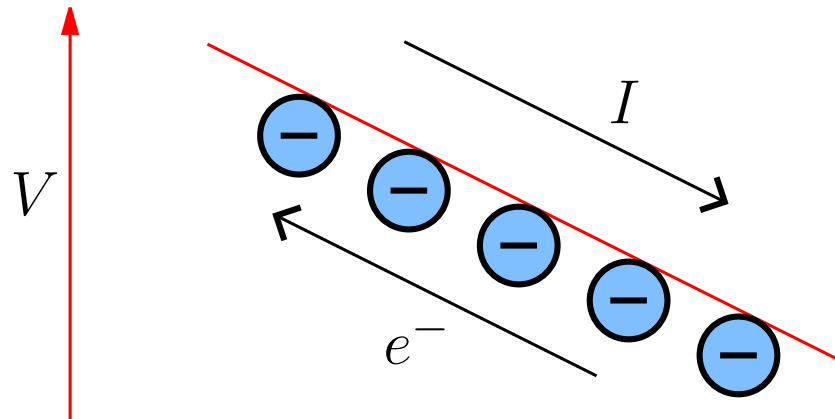- Current said to flow from high potential to low (historical).
- Actually, electrons flowing from low to high.



- Doesn't matter, except in rare cases.

Ohm's law [Text: Sect. 25-3]

● **Definition:** *Ohm's law*

Ohm's law [Text: Sect. 25-3]

● **Definition:** *Ohm's law*

- Current I proportional to voltage difference V that caused it, $V \propto I$, or

$$V = IR.$$

Ohm's law [Text: Sect. 25-3]

● **Definition:** *Ohm's law*

- Current I proportional to voltage difference V that caused it, $V \propto I$, or

$$V = IR.$$

- R is proportionality constant, called **resistance**.

Ohm's law [Text: Sect. 25-3]

● Definition: *Ohm's law*

- Current I proportional to voltage difference V that caused it, $V \propto I$, or

$$V = IR.$$

- R is proportionality constant, called **resistance**.
- Water analogy: $\frac{1}{R} \leftrightarrow$ cross-section of pipe (restricts flow).

Ohm's law [Text: Sect. 25-3]

● Definition: *Ohm's law*

- Current I proportional to voltage difference V that caused it, $V \propto I$, or

$$V = IR.$$

- R is proportionality constant, called **resistance**.
- Water analogy: $\frac{1}{R} \leftrightarrow$ cross-section of pipe (restricts flow).
- Ohm's law states R is constant.

Ohm's law [Text: Sect. 25-3]

● Definition: *Ohm's law*

- Current I proportional to voltage difference V that caused it, $V \propto I$, or

$$V = IR.$$

- R is proportionality constant, called **resistance**.
- Water analogy: $\frac{1}{R} \leftrightarrow$ cross-section of pipe (restricts flow).
- Ohm's law states R is constant.
- Not always true (will see in lab).

Ohm's law

- **Unit: Ohm, Ω**

Ohm's law

- **Unit: Ohm, Ω**

- Units of resistance,

$$1 \Omega = 1 \text{ V/A}.$$

Ohm's law

- **Unit: Ohm, Ω**

- Units of resistance,

$$1 \Omega = 1 \text{ V/A.}$$

- **Definition: *Resistor***

Ohm's law

- **Unit: Ohm, Ω**

- Units of resistance,

$$1 \Omega = 1 \text{ V/A.}$$

- **Definition: *Resistor***

- A circuit component that obeys Ohm's law.

Ohm's law

- **Unit: Ohm, Ω**

- Units of resistance,

$$1 \Omega = 1 \text{ V/A.}$$

- **Definition: *Resistor***

- A circuit component that obeys Ohm's law.
- Has a specific resistance, R .


Ohm's law

- **Unit: Ohm, Ω**

- Units of resistance,

$$1 \Omega = 1 \text{ V/A.}$$

- **Definition: *Resistor***

- A circuit component that obeys Ohm's law.
- Has a specific resistance, R .
- Circuit diagram symbol: 


Ohm's law

● Unit: Ohm, Ω

- Units of resistance,


$$1 \Omega = 1 \text{ V/A.}$$

● Definition: *Resistor*

- A circuit component that obeys Ohm's law.
- Has a specific resistance, R .
- Circuit diagram symbol: 
- R depends on material, size, shape, etc.


Resistivity [Text: Sect. 25-4]

● **Definition:** *Resistivity*, ρ

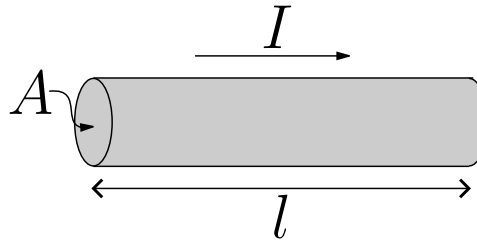

Resistivity [Text: Sect. 25-4]

- **Definition:** *Resistivity*, ρ

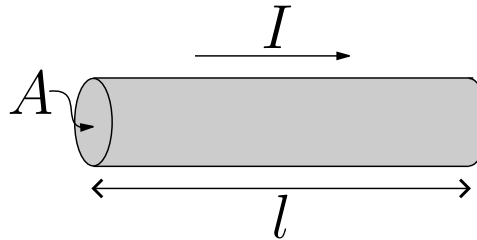


- Empirically found that metals obey

$$R = \rho \frac{l}{A}.$$

Resistivity [Text: Sect. 25-4]

- **Definition:** *Resistivity*, ρ

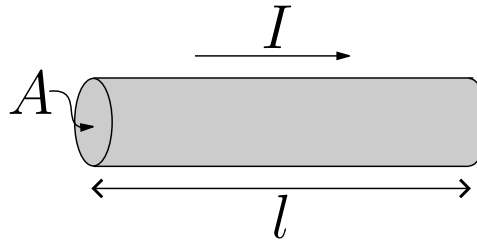


- Empirically found that metals obey

$$R = \rho \frac{l}{A}.$$

- Proportionality constant, ρ , depends on material and temperature, not much else.

Resistivity [Text: Sect. 25-4]

- **Definition:** *Resistivity*, ρ

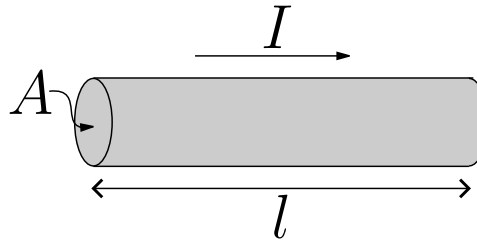

- Empirically found that metals obey

$$R = \rho \frac{l}{A}.$$

- Proportionality constant, ρ , depends on material and temperature, not much else.

- **Interactive Quiz: PRS 08c**

End

● Practice Problems:

- Ch. 24: Q. 3, 7, 9, 13, 17.
- Ch. 24: Pr. 1, 3, 5, 7, 9, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 39, 41, 43, 45, 47, 51, 53, 55, 57, 59, 67, 69, 71, 73, 75, 77, 81, 83, 85, 87.

End

● Practice Problems:

- Ch. 24: Q. 3, 7, 9, 13, 17.
- Ch. 24: Pr. 1, 3, 5, 7, 9, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 39, 41, 43, 45, 47, 51, 53, 55, 57, 59, 67, 69, 71, 73, 75, 77, 81, 83, 85, 87.

● Midterm Test: #2

End

● Practice Problems:

- Ch. 24: Q. 3, 7, 9, 13, 17.
- Ch. 24: Pr. 1, 3, 5, 7, 9, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 39, 41, 43, 45, 47, 51, 53, 55, 57, 59, 67, 69, 71, 73, 75, 77, 81, 83, 85, 87.

● Midterm Test: #2

- Second 60 min. test on Mon (Jul 14).

End

● Practice Problems:

- Ch. 24: Q. 3, 7, 9, 13, 17.
- Ch. 24: Pr. 1, 3, 5, 7, 9, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 39, 41, 43, 45, 47, 51, 53, 55, 57, 59, 67, 69, 71, 73, 75, 77, 81, 83, 85, 87.

● Midterm Test: #2

- Second 60 min. test on Mon (Jul 14).
- Will cover all material in Lectures 4–8 (except Ch. 25).

End

● Practice Problems:

- Ch. 24: Q. 3, 7, 9, 13, 17.
- Ch. 24: Pr. 1, 3, 5, 7, 9, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 39, 41, 43, 45, 47, 51, 53, 55, 57, 59, 67, 69, 71, 73, 75, 77, 81, 83, 85, 87.

● Midterm Test: #2

- Second 60 min. test on Mon (Jul 14).
- Will cover all material in Lectures 4–8 (except Ch. 25).

● Interactive Quiz: Feedback

End

● Practice Problems:

- Ch. 24: Q. 3, 7, 9, 13, 17.
- Ch. 24: Pr. 1, 3, 5, 7, 9, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 39, 41, 43, 45, 47, 51, 53, 55, 57, 59, 67, 69, 71, 73, 75, 77, 81, 83, 85, 87.

● Midterm Test: #2

- Second 60 min. test on Mon (Jul 14).
- Will cover all material in Lectures 4–8 (except Ch. 25).

● Interactive Quiz: Feedback

● Tutorial Question: tut08