### UBC Physics 102 Lecture 10

**Rik Blok** 



### Outline

- ⊳ Emf
- Resistors in series and parallel
- ▷ Kirchhoff's rules
- ⊳ RC Circuits
- ⊳ End



#### **Definition:** Emf, $\mathscr{E}$



#### • Definition: Emf, $\mathscr{E}$

Theoretical maximum voltage gain of battery.



### **Definition:** Emf, $\mathscr{E}$

- Theoretical maximum voltage gain of battery.
- Historically called *electromotive force* but is actually a voltage not a force.



### **Definition:** Emf, $\mathscr{E}$

- Theoretical maximum voltage gain of battery.
- Historically called *electromotive force* but is actually a voltage not a force.

#### Discussion: Batteries



### **Definition:** Emf, $\mathscr{E}$

- Theoretical maximum voltage gain of battery.
- Historically called *electromotive force* but is actually a voltage not a force.

#### Discussion: Batteries

• Batteries have internal resistance,  $r_{int}$ .



### **Definition:** Emf, $\mathscr{E}$

- Theoretical maximum voltage gain of battery.
- Historically called *electromotive force* but is actually a voltage not a force.

#### Discussion: Batteries

- Batteries have internal resistance, r<sub>int</sub>.
- Some voltage loss across  $r_{int}$ .





#### Discussion: Batteries, contd



#### Discussion: Batteries, contd

When current I flowing net voltage across terminals is

$$V = \mathscr{E} - r_{int}I.$$



#### Discussion: Batteries, contd

 When current I flowing net voltage across terminals is

$$V = \mathscr{E} - r_{int}I.$$

•  $\mathscr{E}$  and  $r_{int}$  properties of battery (Lab 3).



#### Discussion: Batteries, contd

 When current I flowing net voltage across terminals is

$$V = \mathscr{E} - r_{int}I.$$

- $\mathscr{E}$  and  $r_{int}$  properties of battery (Lab 3).
- In problems you may see & instead of V. Assume no internal resistance.



Derivation: Resistors in series





Derivation: Resistors in series



 No branches so same current goes through both resistors.



Derivation: Resistors in series



- No branches so same current goes through both resistors.
- Voltage drop across each resistor:  $V_1 = IR_1$ ,  $V_2 = IR_2$ .



Derivation: Resistors in series



- No branches so same current goes through both resistors.
- Voltage drop across each resistor:  $V_1 = IR_1$ ,  $V_2 = IR_2$ .
- Voltage drop must equal voltage gain of battery,

$$V = V_1 + V_2 \\ = I(R_1 + R_2).$$

http://www.zoology.ubc.ca/~rikblok/phys102/lecture/

Derivation: Resistors in series, contd



Derivation: Resistors in series, contd

• From Ohm's law V = IR resistors in series equivalent to one resistor with resistance

$$R_{eq} = R_1 + R_2 + \cdots.$$



Derivation: Resistors in parallel





Derivation: Resistors in parallel



• Voltage drop must be same across both paths so,  $I_1 = \frac{V}{R_1}$ ,  $I_2 = \frac{V}{R_2}$ .



Derivation: Resistors in parallel



- Voltage drop must be same across both paths so,  $I_1 = \frac{V}{R_1}$ ,  $I_2 = \frac{V}{R_2}$ .
- Current splits across branch,

$$I = I_1 + I_2$$
$$= V\left(\frac{1}{R_1} + \frac{1}{R_2}\right) = \frac{V}{R_{eq}}$$



Derivation: Resistors in parallel, contd



### Derivation: Resistors in parallel, contd

• Resistors in parallel equivalent to one resistor with resistance  $R_{eq}$ , where

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}.$$



### Derivation: Resistors in parallel, contd

• Resistors in parallel equivalent to one resistor with resistance  $R_{eq}$ , where

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}.$$

 Can simplify (most) complex circuits by replacing series and parallel combinations by equivalents.



### Derivation: Resistors in parallel, contd

• Resistors in parallel equivalent to one resistor with resistance  $R_{eq}$ , where

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}.$$

- Can simplify (most) complex circuits by replacing series and parallel combinations by equivalents.
- Interactive Quiz: PRS 10a



Example: Pr. 11



#### **Example: Pr. 11**

What is the net resistance of the circuit connected to the battery as shown?





#### **Example: Pr. 11**

What is the net resistance of the circuit connected to the battery as shown?



Solution: Pr. 11



### **Example: Pr. 11**

What is the net resistance of the circuit connected to the battery as shown?



#### Solution: Pr. 11

 To simplify the circuit we need to find a set of resistors in series or parallel.



Solution: Pr. 11, contd



#### Solution: Pr. 11, contd

• 2 in series at the bottom right, the equivalent resistance is  $R_1 = 2R$ .





#### Solution: Pr. 11, contd

• 2 in series at the bottom right, the equivalent resistance is  $R_1 = 2R$ .



• Parallel:  $\frac{1}{R_2} = \frac{1}{R} + \frac{1}{2R}$ , or  $R_2 = \frac{2}{3}R$ .





Solution: Pr. 11, contd



Solution: Pr. 11, contd

• Series: 
$$R_3 = \frac{5}{3}R$$
.





Solution: Pr. 11, contd

• Series: 
$$R_3 = \frac{5}{3}R$$
.



• Parallel:  $\frac{1}{R_4} = \frac{1}{R} + \frac{3}{5R}$ , or  $R_4 = \frac{5}{8}R$ .





Solution: Pr. 11, contd


# **Resistors in series and parallel, contd**

Solution: Pr. 11, contd

• Series: 
$$R_5 = \frac{13}{8}R$$
.





# **Resistors in series and parallel, contd**

Solution: Pr. 11, contd

• Series: 
$$R_5 = \frac{13}{8}R$$
.



• So the net resistance is  $R_5 = \frac{13}{8}R$ .



#### Discussion: Kirchhoff's rules



### Discussion: Kirchhoff's rules

Can't simplify every combination. For example:





### Discussion: Kirchhoff's rules

Can't simplify every combination. For example:



Can't isolate any parallel or series combinations.



### Discussion: Kirchhoff's rules

Can't simplify every combination. For example:



- Can't isolate any parallel or series combinations.
- Have to go back to basics.



**Definition:** *Kirchhoff's branch rule* 



#### Definition: Kirchhoff's branch rule

At a branch



$$\sum I_{in} = \sum I_{out}.$$



### Definition: Kirchhoff's branch rule

At a branch



$$\sum I_{in} = \sum I_{out}.$$

Follows from conservation of charge.



### Definition: Kirchhoff's branch rule

At a branch



$$\sum I_{in} = \sum I_{out}.$$

- Follows from conservation of charge.
- Hint: sometimes you don't know the direction of the current. Then just guess and work out the answer. If I < 0 then you know it's going the other direction.</p>



Definition: Kirchhoff's loop rule



### Definition: Kirchhoff's loop rule

Around a loop



$$\sum V = 0.$$



### Definition: Kirchhoff's loop rule

Around a loop



$$\sum V = 0.$$

Follows from conservation of energy.



### Definition: Kirchhoff's loop rule

Around a loop



$$\sum V = 0.$$

- Follows from conservation of energy.
- Interactive Quiz: PRS 10b



Discussion: Combinations of batteries



### Discussion: Combinations of batteries

 Batteries can be arranged in series, parallel, or even opposition (head to head).



### Discussion: Combinations of batteries

- Batteries can be arranged in series, parallel, or even opposition (head to head).
- Rule: voltage gain if battery inline with current (current goes from – battery terminal to +). Voltage drop if battery reversed (opposes current).



### Discussion: Combinations of batteries

- Batteries can be arranged in series, parallel, or even opposition (head to head).
- Rule: voltage gain if battery inline with current (current goes from – battery terminal to +). Voltage drop if battery reversed (opposes current).
- Kirchhoff's rules apply.



### Discussion: Combinations of batteries

- Batteries can be arranged in series, parallel, or even opposition (head to head).
- Rule: voltage gain if battery inline with current (current goes from – battery terminal to +). Voltage drop if battery reversed (opposes current).
- Kirchhoff's rules apply.

#### Interactive Quiz: PRS 10c





#### Discussion: RC Circuits

Circuits can contain both resistors and capacitors.



- Circuits can contain both resistors and capacitors.
- Resistors limit current so it takes time for charge to build up on capacitor.



- Circuits can contain both resistors and capacitors.
- Resistors limit current so it takes time for charge to build up on capacitor.
- In steady state no current through capacitor.



- Circuits can contain both resistors and capacitors.
- Resistors limit current so it takes time for charge to build up on capacitor.
- In steady state no current through capacitor.
- Current decays exponentially over time,

$$I(t) = I_0 e^{-t/\tau}.$$



#### Discussion: RC Circuits, contd





### Discussion: RC Circuits, contd



• au is time it takes for current to drop close (about  $\frac{2}{3}$  of the way) to zero.

UBC

Discussion: RC Circuits, contd



### Discussion: RC Circuits, contd

• Current is rate of change of charge on capacitor so charge (and voltage,  $V = \frac{Q}{C}$ ) approach final value exponentially,

$$Q(t) - Q_{\infty} = (Q_0 - Q_{\infty})e^{-t/\tau},$$
  
 $V(t) - V_{\infty} = (V_0 - V_{\infty})e^{-t/\tau}.$ 



### Discussion: RC Circuits, contd

• Current is rate of change of charge on capacitor so charge (and voltage,  $V = \frac{Q}{C}$ ) approach final value exponentially,

$$Q(t) - Q_{\infty} = (Q_0 - Q_{\infty})e^{-t/\tau},$$
  
 $V(t) - V_{\infty} = (V_0 - V_{\infty})e^{-t/\tau}.$ 

• Use what you know about initial conditions and steady states to find  $I_0$ ,  $Q_0$ ,  $V_0$ ,  $Q_\infty$ , and  $V_\infty$ .



**• Definition:** Time constant,  $\tau$ 



#### **Definition:** Time constant, $\tau$

 In simple circuits, with just one capacitor and one resistor in series,

$$\tau = RC.$$



#### **Definition:** Time constant, $\tau$

 In simple circuits, with just one capacitor and one resistor in series,

$$\tau = RC.$$

 Doesn't hold if more capacitors or resistors. But may be able to simplify using series/parallel rules.



#### **Definition:** Time constant, $\tau$

 In simple circuits, with just one capacitor and one resistor in series,

$$\tau = RC.$$

- Doesn't hold if more capacitors or resistors. But may be able to simplify using series/parallel rules.
- Example: Charging a capacitor



#### **Definition:** Time constant, $\tau$

 In simple circuits, with just one capacitor and one resistor in series,

$$\tau = RC.$$

 Doesn't hold if more capacitors or resistors. But may be able to simplify using series/parallel rules.

### **•** Example: Charging a capacitor

In a circuit with a battery &, resistor R, and capacitor C (initially uncharged) in series, what is the current I as a function of time?



Solution: Charging a capacitor





Solution: Charging a capacitor



• In this simple circuit the time constant is  $\tau = RC$ .


Solution: Charging a capacitor



- In this simple circuit the time constant is  $\tau = RC$ .
- We know  $I(t) = I_0 e^{-t/\tau}$  so we need to find  $I_0$ .



### Solution: Charging a capacitor



- In this simple circuit the time constant is  $\tau = RC$ .
- We know  $I(t) = I_0 e^{-t/\tau}$  so we need to find  $I_0$ .
- I<sub>0</sub> is the current at the instant the capacitor starts charging (when the switch S is closed).



### Solution: Charging a capacitor



- In this simple circuit the time constant is  $\tau = RC$ .
- We know  $I(t) = I_0 e^{-t/\tau}$  so we need to find  $I_0$ .
- I<sub>0</sub> is the current at the instant the capacitor starts charging (when the switch S is closed).
- Initially the capacitor is uncharged,  $Q_0 = 0$ . So  $V_0 = \frac{Q_0}{C} = 0$ .



Solution: Charging a capacitor, contd



### Solution: Charging a capacitor, contd

• Then the only voltage drop in the circuit is the resistor,  $V = I_0 R$ , and from Kirchhoff's loop rule,

$$\mathscr{E} = I_0 R.$$



### Solution: Charging a capacitor, contd

• Then the only voltage drop in the circuit is the resistor,  $V = I_0 R$ , and from Kirchhoff's loop rule,

 $\mathscr{E} = I_0 R.$ 

• So  $I_0 = \frac{\mathscr{E}}{R}$  and the current as a function of time is

$$I(t) = \frac{\mathscr{E}}{R}e^{-t/(RC)}. \quad \Box$$



Solution: Charging a capacitor, contd

• Then the only voltage drop in the circuit is the resistor,  $V = I_0 R$ , and from Kirchhoff's loop rule,

 $\mathscr{E} = I_0 R.$ 

• So  $I_0 = \frac{\mathscr{E}}{R}$  and the current as a function of time is

$$I(t) = \frac{\mathscr{E}}{R}e^{-t/(RC)}. \quad \Box$$

#### Interactive Quiz: PRS 10d



### End

#### Practice Problems:

- Ch. 26: Q. 3, 7, 9, 11, 13, 15, 17, 19.
- Ch. 26: Pr. 1, 3, 5, 7, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 41, 43, 45, 63, 65, 67, 69, 71, 73, 75, 77, 79, 81, 83.



### End

#### Practice Problems:

- Ch. 26: Q. 3, 7, 9, 11, 13, 15, 17, 19.
- Ch. 26: Pr. 1, 3, 5, 7, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 41, 43, 45, 63, 65, 67, 69, 71, 73, 75, 77, 79, 81, 83.
- Interactive Quiz: Feedback



### End

#### Practice Problems:

- Ch. 26: Q. 3, 7, 9, 11, 13, 15, 17, 19.
- Ch. 26: Pr. 1, 3, 5, 7, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 41, 43, 45, 63, 65, 67, 69, 71, 73, 75, 77, 79, 81, 83.
- Interactive Quiz: Feedback
- Tutorial Question: tut10

