

UBC Physics 102

Lecture 15

Rik Blok



Outline

- ▷ AC source
- ▷ R circuits
- ▷ L circuits
- ▷ C circuits
- ▷ LRC circuits
- ▷ Resonance
- ▷ End

AC source [Text: Sect. 31-1]

● **Definition:** *AC source*

AC source [Text: Sect. 31-1]

● **Definition:** *AC source*

- Generates an alternating (sinusoidal unless otherwise stated) current,

$$I = I_0 \sin \omega t.$$

AC source [Text: Sect. 31-1]

● Definition: AC source

- Generates an alternating (sinusoidal unless otherwise stated) current,

$$I = I_0 \sin \omega t.$$

- Angular frequency ω related to frequency f and period T by

$$\omega = 2\pi f = \frac{2\pi}{T}.$$

AC source [Text: Sect. 31-1]

● Definition: AC source

- Generates an alternating (sinusoidal unless otherwise stated) current,

$$I = I_0 \sin \omega t.$$

- Angular frequency ω related to frequency f and period T by

$$\omega = 2\pi f = \frac{2\pi}{T}.$$

- Circuit symbol: 

AC source [Text: Sect. 31-1]

● Definition: AC source

- Generates an alternating (sinusoidal unless otherwise stated) current,

$$I = I_0 \sin \omega t.$$

- Angular frequency ω related to frequency f and period T by


$$\omega = 2\pi f = \frac{2\pi}{T}.$$

- Circuit symbol: 

- Note: multimeters read RMS values, not peak.


R circuits [Text: Sect. 31-2]

● Discussion: R circuits


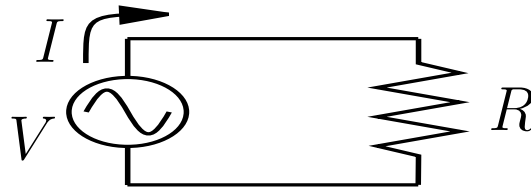


R circuits [Text: Sect. 31-2]

● Discussion: R circuits

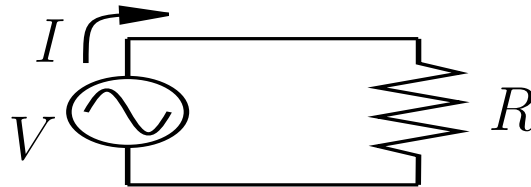

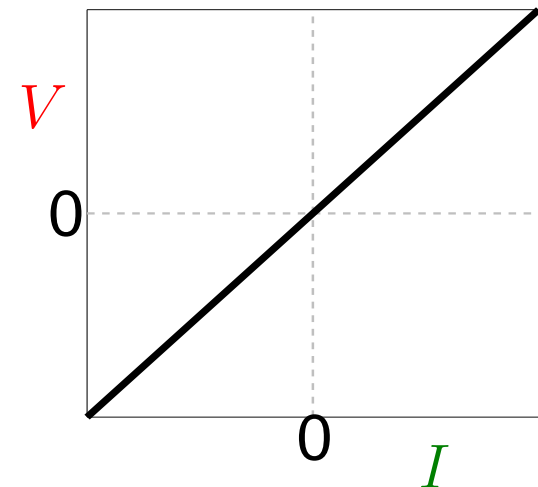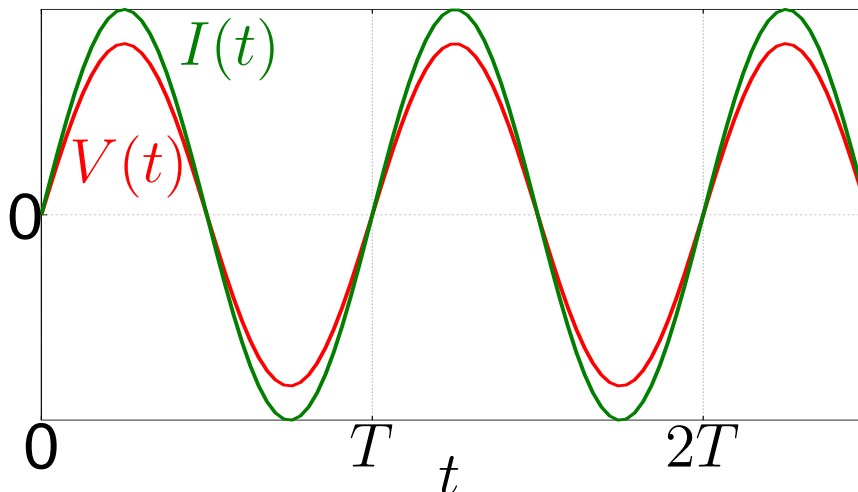- Voltage drop across resistor, $V = IR = I_0 R \sin \omega t$ so voltage amplitude is $V_0 = I_0 R$.



L circuits [Text: Sect. 31-3]

● Discussion: R circuits, contd

L circuits [Text: Sect. 31-3]

● Discussion: R circuits, contd

- RMS voltage, $V_{\text{RMS}} = I_{\text{RMS}} R$.

L circuits [Text: Sect. 31-3]


- **Discussion: R circuits, contd**

- RMS voltage, $V_{\text{RMS}} = I_{\text{RMS}} R$.

- **Interactive Quiz: PRS 15a**

L circuits [Text: Sect. 31-3]

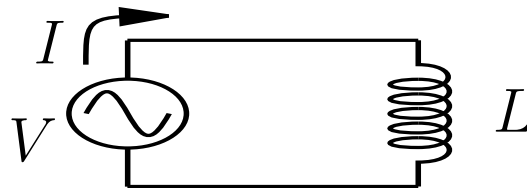- **Discussion: R circuits, contd**
 - RMS voltage, $V_{\text{RMS}} = I_{\text{RMS}} R$.
- **Interactive Quiz: PRS 15a**
- **Discussion: L circuits**




L circuits [Text: Sect. 31-3]

- **Discussion: R circuits, contd**

- RMS voltage, $V_{\text{RMS}} = I_{\text{RMS}} R$.

- **Interactive Quiz: PRS 15a**

- **Discussion: L circuits**

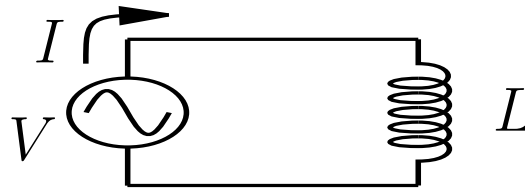

- By Kirchhoff's loop rule,

$$\begin{aligned} V &= L \frac{dI}{dt} = L \frac{d}{dt} I_0 \sin \omega t \\ &= \omega L I_0 \cos \omega t. \end{aligned}$$



L circuits, contd

● Discussion: L circuits, contd

L circuits, contd

● Discussion: L circuits, contd

- Current *lags* voltage by 90° .

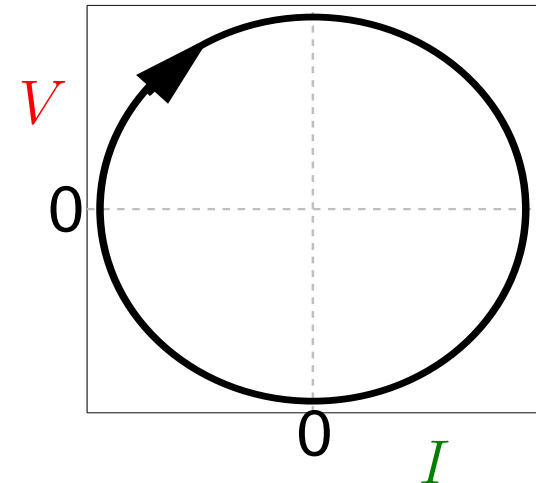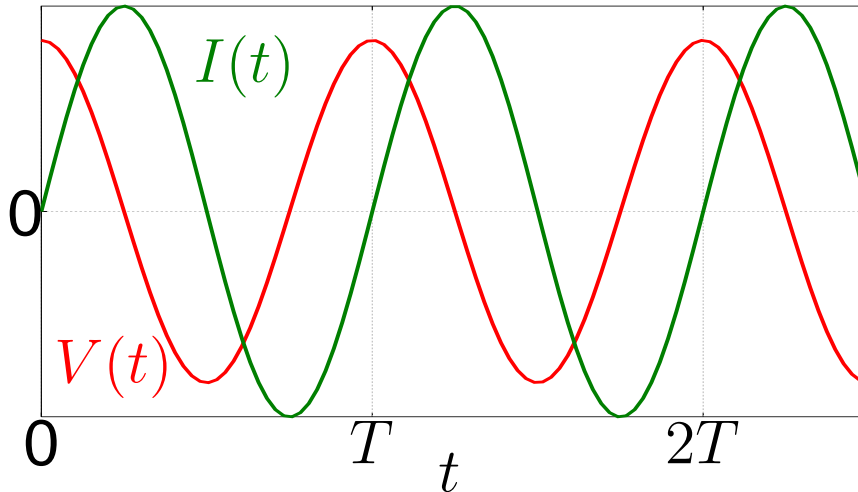

L circuits, contd

- **Definition:** *Inductive reactance*, X_L

L circuits, contd

- **Definition:** *Inductive reactance*, X_L
 - Voltage amplitude is $V_0 = \omega L I_0$.

L circuits, contd

- **Definition:** *Inductive reactance*, X_L
 - Voltage amplitude is $V_0 = \omega L I_0$.
 - Multimeter will give readings $V_{\text{RMS}} = I_{\text{RMS}} X_L$ where

$$X_L = \omega L.$$

L circuits, contd

- **Definition:** *Inductive reactance*, X_L
 - Voltage amplitude is $V_0 = \omega L I_0$.
 - Multimeter will give readings $V_{\text{RMS}} = I_{\text{RMS}} X_L$ where

$$X_L = \omega L.$$

- X_L called inductive *reactance*.

L circuits, contd


- **Definition:** *Inductive reactance*, X_L
 - Voltage amplitude is $V_0 = \omega L I_0$.
 - Multimeter will give readings $V_{\text{RMS}} = I_{\text{RMS}} X_L$ where

$$X_L = \omega L.$$

- X_L called inductive *reactance*.
- Like resistance except current out of phase with voltage.


C circuits [Text: Sect. 31-4]

● Discussion: C circuits

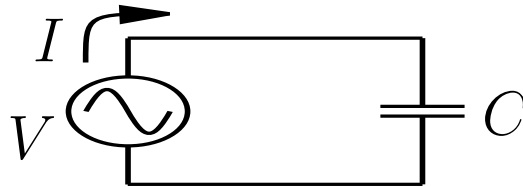

C circuits [Text: Sect. 31-4]


• Discussion: C circuits

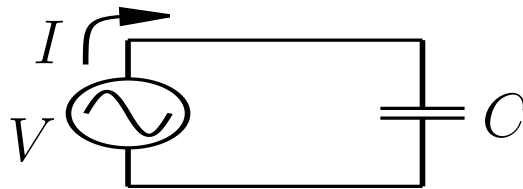

- By Kirchhoff's loop rule, $V = \frac{Q}{C}$.

C circuits [Text: Sect. 31-4]

Discussion: C circuits

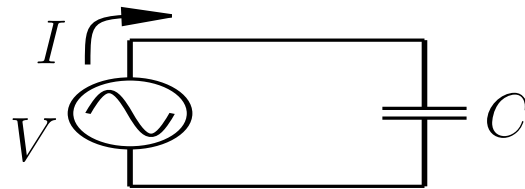


- By Kirchhoff's loop rule, $V = \frac{Q}{C}$.
- How does this relate to current? $I = \frac{dQ}{dt}$ so

$$\frac{dV}{dt} = \frac{I}{C} = \frac{I_0}{C} \sin \omega t.$$

C circuits [Text: Sect. 31-4]

Discussion: C circuits

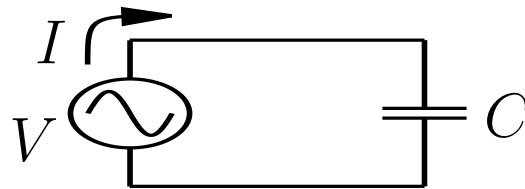

- By Kirchhoff's loop rule, $V = \frac{Q}{C}$.
- How does this relate to current? $I = \frac{dQ}{dt}$ so

$$\frac{dV}{dt} = \frac{I}{C} = \frac{I_0}{C} \sin \omega t.$$

- Solution is

$$V = -\frac{I_0}{\omega C} \cos \omega t.$$



C circuits, contd

● Discussion: C circuits, contd

C circuits, contd

● Discussion: C circuits, contd

- Current *leads* voltage by 90° .

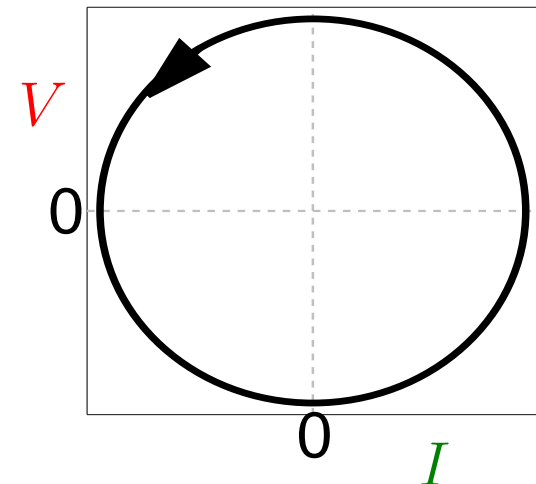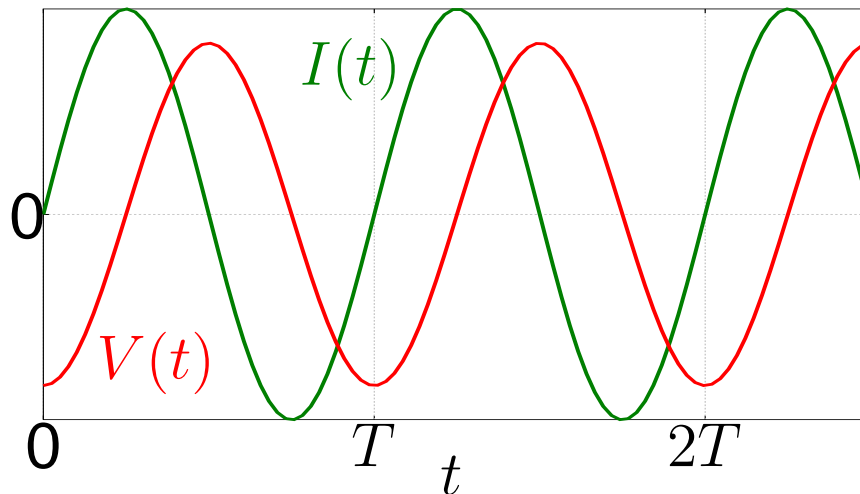

C circuits, contd

- **Definition:** *Capacitive reactance*, X_C

C circuits, contd

- **Definition:** *Capacitive reactance*, X_C
 - Voltage amplitude is $V_0 = \frac{I_0}{\omega C}$.

C circuits, contd

- **Definition:** *Capacitive reactance*, X_C
 - Voltage amplitude is $V_0 = \frac{I_0}{\omega C}$.
 - Multimeter will give readings $V_{\text{RMS}} = I_{\text{RMS}} X_C$ where

$$X_C = \frac{1}{\omega C}.$$

C circuits, contd

- **Definition:** *Capacitive reactance*, X_C

- Voltage amplitude is $V_0 = \frac{I_0}{\omega C}$.
- Multimeter will give readings $V_{\text{RMS}} = I_{\text{RMS}} X_C$ where

$$X_C = \frac{1}{\omega C}.$$

- X_C called inductive *reactance*.

C circuits, contd

- **Definition:** *Capacitive reactance*, X_C

- Voltage amplitude is $V_0 = \frac{I_0}{\omega C}$.
- Multimeter will give readings $V_{\text{RMS}} = I_{\text{RMS}} X_C$ where

$$X_C = \frac{1}{\omega C}.$$

- X_C called inductive *reactance*.

- **Discussion: CIVIL memory aid**

C circuits, contd

- **Definition:** *Capacitive reactance*, X_C

- Voltage amplitude is $V_0 = \frac{I_0}{\omega C}$.
- Multimeter will give readings $V_{\text{RMS}} = I_{\text{RMS}} X_C$ where

$$X_C = \frac{1}{\omega C}.$$

- X_C called inductive *reactance*.

- **Discussion: CIVIL memory aid**

- CIVIL = in Capacitors I comes before V.

C circuits, contd

- **Definition:** *Capacitive reactance*, X_C

- Voltage amplitude is $V_0 = \frac{I_0}{\omega C}$.
- Multimeter will give readings $V_{\text{RMS}} = I_{\text{RMS}} X_C$ where

$$X_C = \frac{1}{\omega C}.$$


- X_C called inductive *reactance*.

- **Discussion: CIVIL memory aid**

- CIVIL = in Capacitors I comes before V.
- CIVIL = V comes before I in inductors (L).


LRC circuits [Text: Sect. 31-5]

● Discussion: LRC circuits

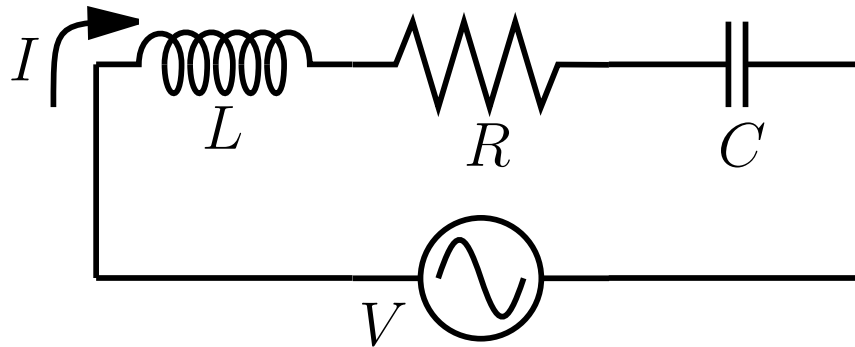

LRC circuits [Text: Sect. 31-5]


● Discussion: LRC circuits

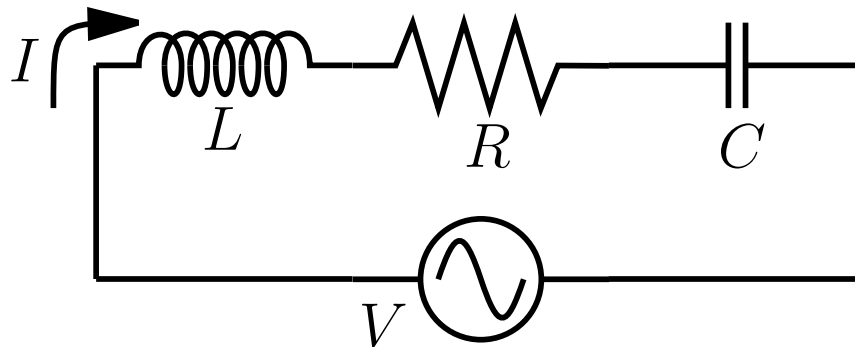

- What if circuit contains all three components in series?

LRC circuits [Text: Sect. 31-5]


● Discussion: LRC circuits

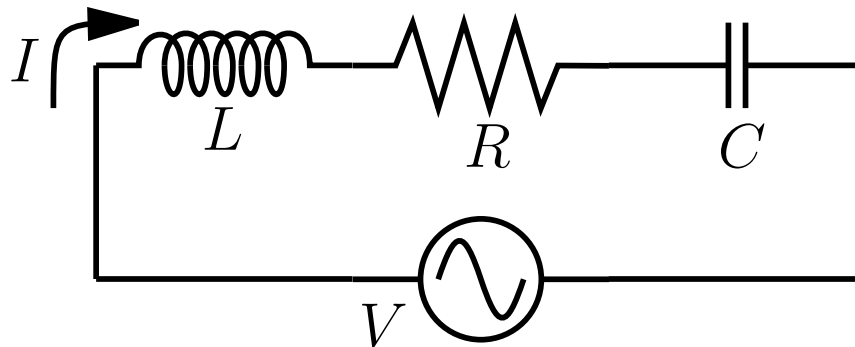

- What if circuit contains all three components in series?
- Same current $I = I_0 \sin \omega t$ goes through each.

LRC circuits [Text: Sect. 31-5]


● Discussion: LRC circuits

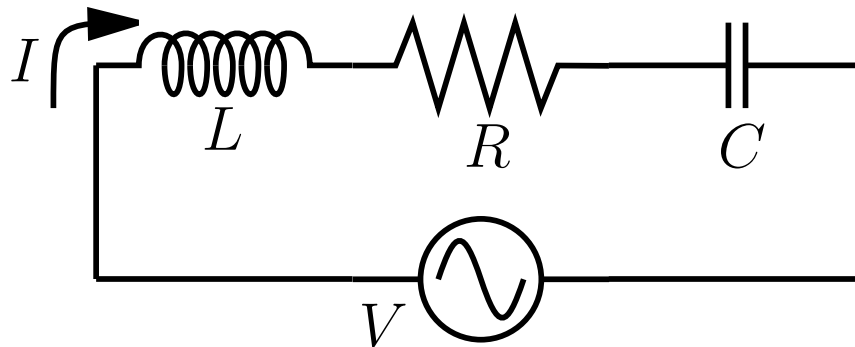

- What if circuit contains all three components in series?
- Same current $I = I_0 \sin \omega t$ goes through each.
- Expect total voltage drop to be $V = V_0 \sin(\omega t + \phi)$.

LRC circuits [Text: Sect. 31-5]


● Discussion: LRC circuits

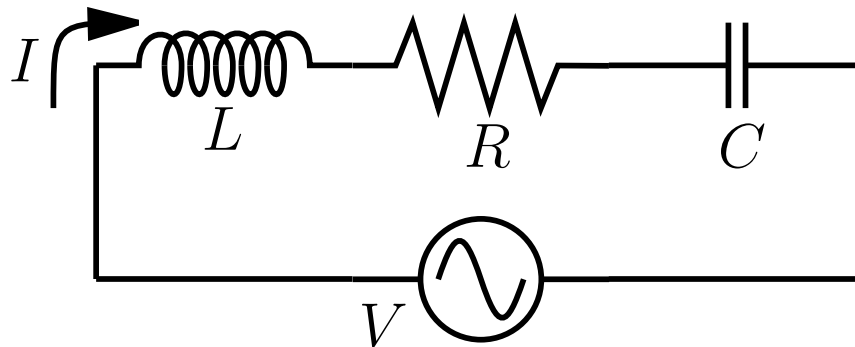

- What if circuit contains all three components in series?
- Same current $I = I_0 \sin \omega t$ goes through each.
- Expect total voltage drop to be $V = V_0 \sin(\omega t + \phi)$.
- But which ϕ ? 0° , $\pm 90^\circ$ or something else?

LRC circuits [Text: Sect. 31-5]

● Discussion: LRC circuits

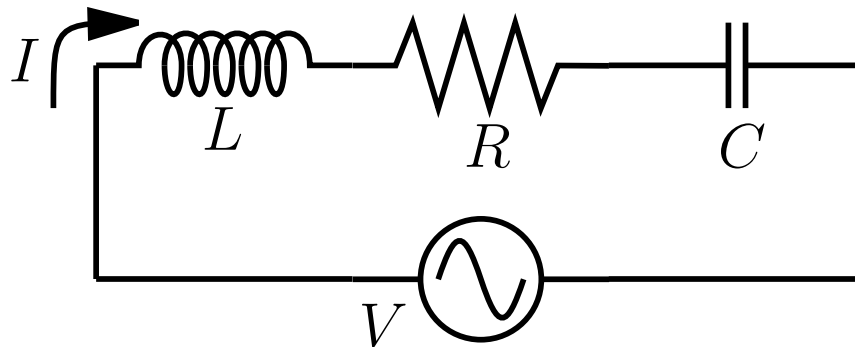

- What if circuit contains all three components in series?
- Same current $I = I_0 \sin \omega t$ goes through each.
- Expect total voltage drop to be $V = V_0 \sin(\omega t + \phi)$.
- But which ϕ ? 0° , $\pm 90^\circ$ or something else?
- And what is V_0 ?

LRC circuits, contd

● Discussion: LRC circuits, contd

LRC circuits, contd

● Discussion: LRC circuits, contd

- From Kirchhoff's loop rule,

$$\begin{aligned} V &= V_R + V_L + V_C \\ &= I_0 R \sin \omega t + I_0 (X_L - X_C) \cos \omega t. \end{aligned}$$

LRC circuits, contd

● Discussion: LRC circuits, contd

- From Kirchhoff's loop rule,

$$\begin{aligned} V &= V_R + V_L + V_C \\ &= I_0 R \sin \omega t + I_0 (X_L - X_C) \cos \omega t. \end{aligned}$$

● Definition: *Impedance*

LRC circuits, contd

● Discussion: LRC circuits, contd

- From Kirchhoff's loop rule,

$$\begin{aligned} V &= V_R + V_L + V_C \\ &= I_0 R \sin \omega t + I_0 (X_L - X_C) \cos \omega t. \end{aligned}$$

● Definition: *Impedance*

- After some geometry (hand waving) we find $V_0 = I_0 Z$.

LRC circuits, contd

● Discussion: LRC circuits, contd

- From Kirchhoff's loop rule,

$$\begin{aligned} V &= V_R + V_L + V_C \\ &= I_0 R \sin \omega t + I_0 (X_L - X_C) \cos \omega t. \end{aligned}$$

● Definition: *Impedance*

- After some geometry (hand waving) we find $V_0 = I_0 Z$.
- Likewise, multimeters will read $V_{\text{RMS}} = I_{\text{RMS}} Z$ where

$$Z = \sqrt{R^2 + (X_L - X_C)^2}.$$

LRC circuits, contd

● **Definition:** *Impedance, contd*

LRC circuits, contd

- **Definition:** *Impedance, contd*

- Z called impedance of circuit.


LRC circuits, contd

- **Definition:** *Impedance, contd*
 - Z called impedance of circuit.
 - “Impedes” current flow like resistance but also phase-shifts it by ϕ .

LRC circuits, contd

● **Definition:** *Impedance, contd*

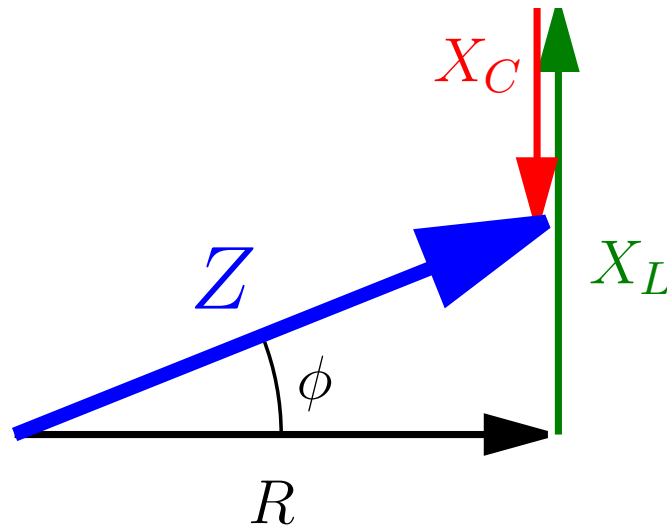- Z called impedance of circuit.
- “Impedes” current flow like resistance but also phase-shifts it by ϕ .
- Vector representation:



LRC circuits, contd

● **Definition:** *Impedance, contd*

LRC circuits, contd

● **Definition:** *Impedance, contd*

● Summary:

Name	Symbol	Phase shift
Resistance	R	0°
Reactance	X	$\pm 90^\circ$
Impedance	Z	ϕ ($ \phi \leq 90^\circ$)

LRC circuits, contd

● **Definition:** *Impedance, contd*

● Summary:

Name	Symbol	Phase shift
Resistance	R	0°
Reactance	X	$\pm 90^\circ$
Impedance	Z	ϕ ($ \phi \leq 90^\circ$)

● **Interactive Quiz: PRS 15b**

LRC circuits, contd

● **Definition:** *Impedance, contd*

● Summary:

Name	Symbol	Phase shift
Resistance	R	0°
Reactance	X	$\pm 90^\circ$
Impedance	Z	ϕ ($ \phi \leq 90^\circ$)

● **Interactive Quiz: PRS 15b**

● **Derivation: Power**

LRC circuits, contd

● **Definition:** *Impedance, contd*

● Summary:

Name	Symbol	Phase shift
Resistance	R	0°
Reactance	X	$\pm 90^\circ$
Impedance	Z	ϕ ($ \phi \leq 90^\circ$)

● **Interactive Quiz: PRS 15b**

● **Derivation: Power**

- L and C don't lose energy, they just swap it back and forth.

LRC circuits, contd

● **Definition:** *Impedance, contd*

● Summary:

Name	Symbol	Phase shift
Resistance	R	0°
Reactance	X	$\pm 90^\circ$
Impedance	Z	ϕ ($ \phi \leq 90^\circ$)

● **Interactive Quiz: PRS 15b**

● **Derivation: Power**

- L and C don't lose energy, they just swap it back and forth.
- Only R loses energy, as heat.

LRC circuits, contd

• Derivation: Power, contd

LRC circuits, contd

• Derivation: Power, contd

- Average rate of power consumption is $\boxed{\overline{P} = I_{\text{RMS}}^2 R}$.

LRC circuits, contd

● Derivation: Power, contd

- Average rate of power consumption is $\boxed{\overline{P} = I_{\text{RMS}}^2 R}$.
- From vector representation we see $R = Z \cos \phi$ so

$$\overline{P} = I_{\text{RMS}}^2 Z \cos \phi = I_{\text{RMS}} V_{\text{RMS}} \cos \phi.$$

LRC circuits, contd

● Derivation: Power, contd

- Average rate of power consumption is $\boxed{\overline{P} = I_{\text{RMS}}^2 R}$.
- From vector representation we see $R = Z \cos \phi$ so

$$\overline{P} = I_{\text{RMS}}^2 Z \cos \phi = I_{\text{RMS}} V_{\text{RMS}} \cos \phi.$$

- $\cos \phi$ called **power factor**.

Resonance [Text: Sect. 31-6]

● Discussion: Resonance

Resonance [Text: Sect. 31-6]

● Discussion: Resonance

- Already saw a LC circuit (without any voltage source) oscillates at frequency $\omega_0 = \frac{1}{\sqrt{LC}}$.

Resonance [Text: Sect. 31-6]

● Discussion: Resonance

- Already saw a LC circuit (without any voltage source) oscillates at frequency $\omega_0 = \frac{1}{\sqrt{LC}}$.
- What is so special about that frequency?

Resonance [Text: Sect. 31-6]

● Discussion: Resonance

- Already saw a LC circuit (without any voltage source) oscillates at frequency $\omega_0 = \frac{1}{\sqrt{LC}}$.
- What is so special about that frequency?
- If we “push” an LRC circuit with an AC source at frequency ω_0 ,

$$X_L = \omega_0 L = \sqrt{\frac{L}{C}},$$

$$X_C = \frac{1}{\omega_0 C} = \sqrt{\frac{L}{C}}.$$

Resonance [Text: Sect. 31-6]

● Discussion: Resonance

- Already saw a LC circuit (without any voltage source) oscillates at frequency $\omega_0 = \frac{1}{\sqrt{LC}}$.
- What is so special about that frequency?
- If we “push” an LRC circuit with an AC source at frequency ω_0 ,


$$X_L = \omega_0 L = \sqrt{\frac{L}{C}},$$

$$X_C = \frac{1}{\omega_0 C} = \sqrt{\frac{L}{C}}.$$

- So $X_L = X_C$.


Resonance, contd

● Discussion: Resonance, contd

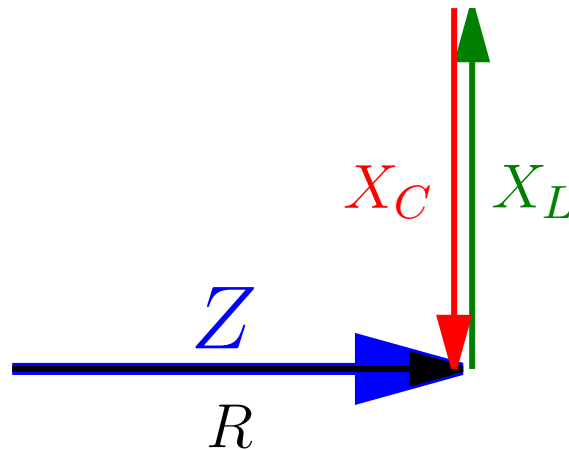

Resonance, contd


• Discussion: Resonance, contd

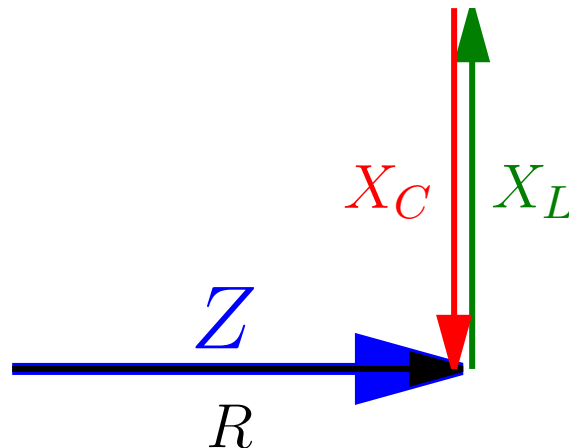

- So $\phi = 0$ and $Z = R$. Changing ω can only make Z bigger.

Resonance, contd

● Discussion: Resonance, contd

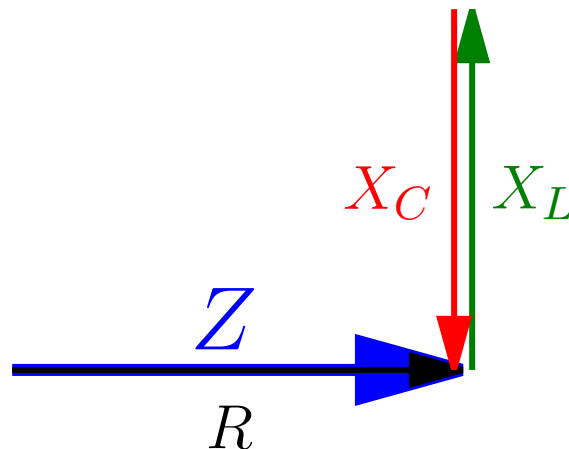

- So $\phi = 0$ and $Z = R$. Changing ω can only make Z bigger.

● Interactive Quiz: PRS 15c

End

● Practice Problems:

- Ch. 31: Q. 1, 3, 5, 7, 9, 11, 13, 15.
- Ch. 31: Pr. 1, 3, 5, 7, 9, 11, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 35, 37, 39, 41, 43, 45, 51, 53.

End

● Practice Problems:

- Ch. 31: Q. 1, 3, 5, 7, 9, 11, 13, 15.
- Ch. 31: Pr. 1, 3, 5, 7, 9, 11, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 35, 37, 39, 41, 43, 45, 51, 53.

● Interactive Quiz: Feedback

End

● Practice Problems:

- Ch. 31: Q. 1, 3, 5, 7, 9, 11, 13, 15.
- Ch. 31: Pr. 1, 3, 5, 7, 9, 11, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 35, 37, 39, 41, 43, 45, 51, 53.

● Interactive Quiz: Feedback

● Tutorial Question: tut15